

Name of the Student: _____

Max. Marks : 19 Marks

Time : 19 Minutes

Q1.


- (a) When an uncharged capacitor is charged by a **constant** current of $4.5 \mu\text{A}$ for 60 s the pd across it becomes 4.4 V.
- (i) Calculate the capacitance of the capacitor.

capacitance _____ F

(3)

- (ii) The capacitor is charged using the circuit shown in **Figure 1**. The battery emf is 6.0 V and its internal resistance is negligible. In order to keep the current constant at $4.5 \mu\text{A}$, the resistance of the variable resistor R is decreased steadily as the charge on the capacitor increases.

Figure 1

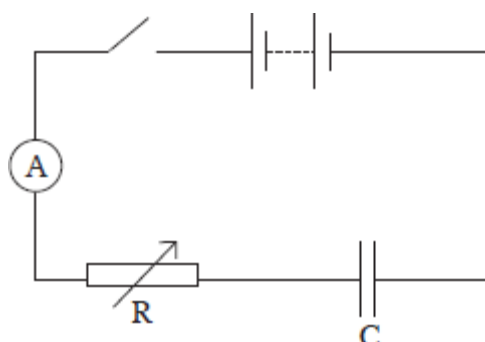


Calculate the resistance of R when the uncharged capacitor has been charging for 30 s.

resistance _____ Ω

(3)

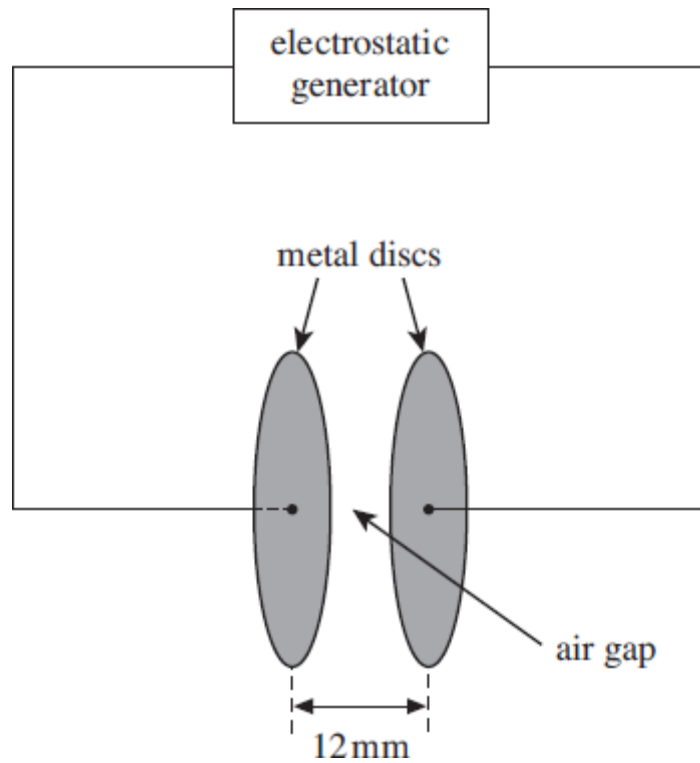- (b) The circuit in **Figure 2** contains a cell, an uncharged capacitor, a fixed resistor and a two-way

large enough for a spark to pass. Sparks are then produced at regular time intervals whilst the generator is switched on.



- (a) The electrostatic generator charges the discs at a constant rate of 3.2×10^{-8} A on a day when the minimum breakdown field strength of the air is 2.5×10^6 V m⁻¹. The discs have a capacitance of 3.7×10^{-12} F.
- (i) The air gap is 12 mm wide. Calculate the minimum pd required across the discs for a spark to occur. Assume that the electric field in the air gap is uniform.

pd _____ V

(1)

- (ii) Calculate the time taken, from when the electrostatic generator is first switched on, for the pd across the discs to reach the value calculated in part (a)(i).

time _____ s

(2)

- (b) The discs are replaced by ones of larger area placed at the same separation, to give a larger

capacitance.

State and explain what effect this increased capacitance will have on:

- (i) the time between consecutive discharges,

(2)

- (ii) the brightness of each spark.

(2)

(Total 7 marks)