

Name of the Student: _____

Max. Marks : 24 Marks


Time : 24 Minutes

Q1.

- (a) A particular heart pacemaker uses a capacitor which has a capacitance of $4.2 \mu\text{F}$. Explain what is meant by a *capacitance of $4.2 \mu\text{F}$* .

(2)

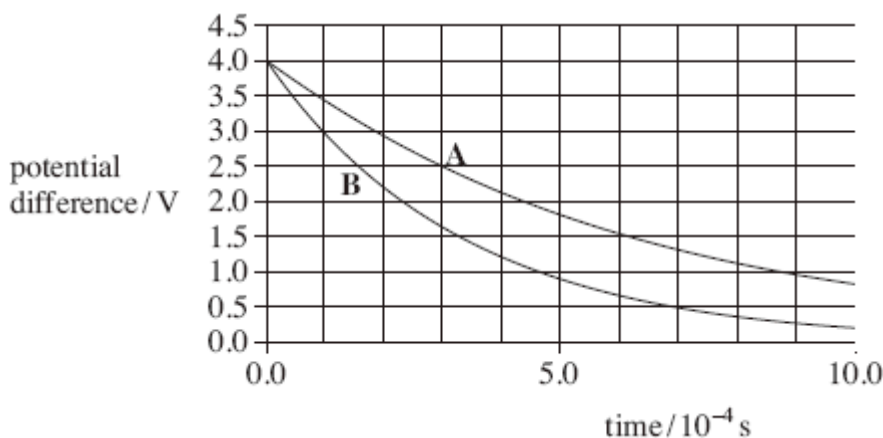- (b) Capacitor **A**, of capacitance $4.2 \mu\text{F}$, is charged to 4.0 V and then discharged through a sample of heart tissue. This capacitor is replaced by capacitor **B** and the charge and discharge process repeated through the same sample of tissue. The discharge curves are shown in the figure below.



- (i) By considering the discharge curve for capacitor **A**, show that the resistance of the sample of heart tissue through which the discharge occurs is approximately 150Ω .

(4)

- (ii) State and explain whether capacitor **B** has a larger or smaller capacitance than that of

capacitor **A**.

(2)

- (c) Capacitor **A** was charged to a potential difference of 4.0V before discharging through the sample of heart tissue. Determine how much energy it passed to the sample of heart tissue in the first 0.90 m s of the discharge.

energy _____ J

(3)

(Total 11 marks)

Q2.

Figure 1 shows a circuit that is used in a defibrillator in which a short pulse of charge is used to revive a patient who suffers a cardiac arrest in which their heart stops beating.

Figure 2 shows how the charge on the capacitor varies with time when the capacitor is charging.

Figure 1


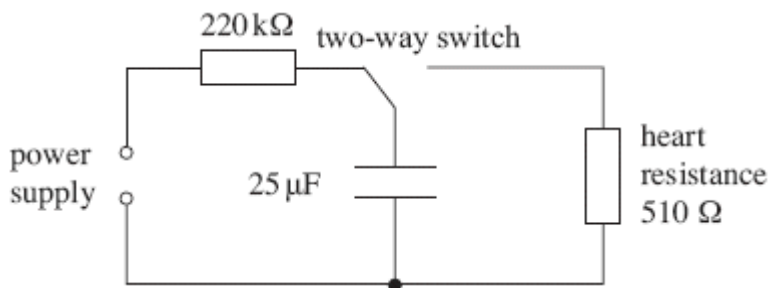


Figure 2

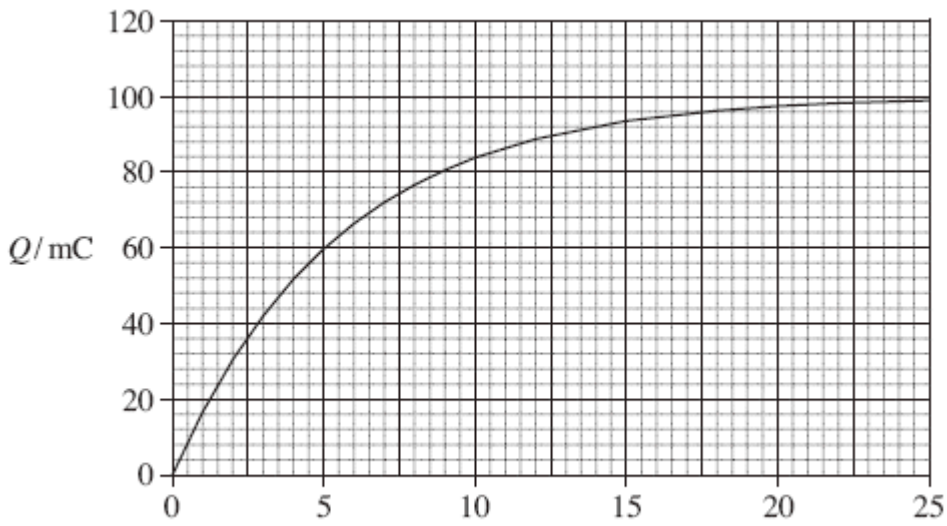

(a) (i) Use **Figure 2** to determine the initial charging current.

initial charging current _____ A

(2)

(ii) Calculate the emf of the supply used to charge the capacitor. Assume that the supply has negligible internal resistance.

emf of the supply _____ V

(2)

(iii) Explain why the current that charges the capacitor falls as the capacitor charges.

(3)

(b) For the system to work successfully, the capacitor has to deliver 140 J of energy to the heart in a pulse that lasts for 10 ms.

(i) Show that the charge on the capacitor when it is storing this much energy is about 85 mC.

(2)

(ii) Calculate the average power supplied during the pulse.

average power _____ W

(1)

(c) The circuit designer suggests that the capacitor can be used successfully after a charging time equal to 1.5 time constants of the charging circuit shown in **Figure 1**.

Explain with a calculation whether or not the designer's suggestion is valid.

(3)

(Total 13 marks)