

Name of the Student: _____

Max. Marks : 23 Marks

Time : 23 Minutes

Q1.

A capacitor of capacitance $330\ \mu\text{F}$ is charged to a potential difference of $9.0\ \text{V}$. It is then discharged through a resistor of resistance $470\ \text{k}\Omega$.

Calculate

- (a) the energy stored by the capacitor when it is fully charged,

(2)

- (b) the time constant of the discharging circuit,

(1)


- (c) the p.d. across the capacitor $60\ \text{s}$ after the discharge has begun.

(3)

(Total 6 marks)

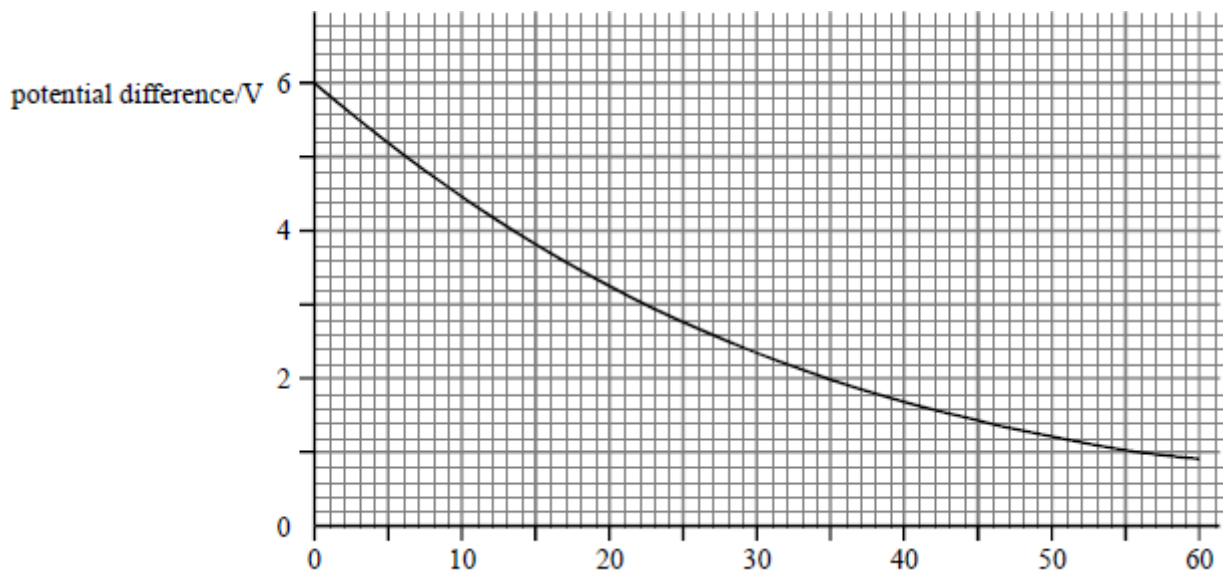Q2.

A student used a voltage sensor connected to a datalogger to plot the discharge curve for a $4.7\ \mu\text{F}$ capacitor. She obtained the following graph.



Use data from the graph to calculate

- (a) the initial charge stored,

(2)

- (b) the energy stored when the capacitor had been discharging for 35 ms,

(3)

- (c) the time constant for the circuit,

(3)

- (d) the resistance of the circuit through which the capacitor was discharging.

(2)

(Total 10 marks)

Q3.

- (a) A $2.0 \mu\text{F}$ capacitor is charged through a resistor from a battery of emf 4.5 V . Sketch a graph on the axes below to show how the charge stored, Q , varies with the potential difference, V , across the capacitor during the charging process. Mark appropriate values on the axes of the

graph.



(2)

(b) (i) Show that the energy stored by a charged capacitor is given by $E = \frac{1}{2}QV$.

(ii) Calculate the energy stored by the capacitor in part (a) when the potential difference across it is 1.5 V.

(5)

(Total 7 marks)