


Name of the Student: _____

Max. Marks : 18 Marks

Time : 18 Minutes

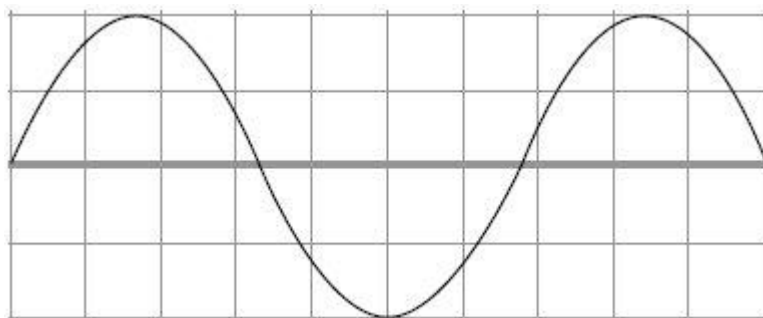Q1.

The diagram below shows an ac waveform that is displayed on an oscilloscope screen.



The time base of the oscilloscope is set at 1.5 ms per division and the y-gain at 1.5 V per division.

(a) For the ac waveform shown,

(i) Calculate the frequency

answer _____ Hz

(3)

(ii) Calculate the peak voltage

answer _____ V

(2)

(iii) the rms voltage

answer _____ V

(2)

(b) State and explain the effect on the oscilloscope trace if the time base is switched off.


(2)

(Total 9 marks)

Q2.


The circuit in **Figure 1** shows a sinusoidal ac source connected to two resistors, R_1 and R_2 , which form a potential divider. Oscilloscope 1 is connected across the source and oscilloscope 2 is connected across R_2 .

Figure 1

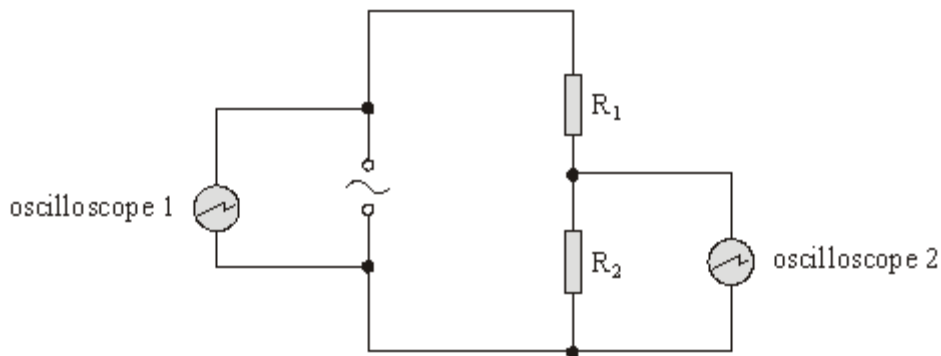

(a) **Figure 2** shows the trace obtained on the screen of oscilloscope 1. The time base of the oscilloscope is set at 10 m/s per division and the voltage sensitivity at 15 V per division.

Figure 2

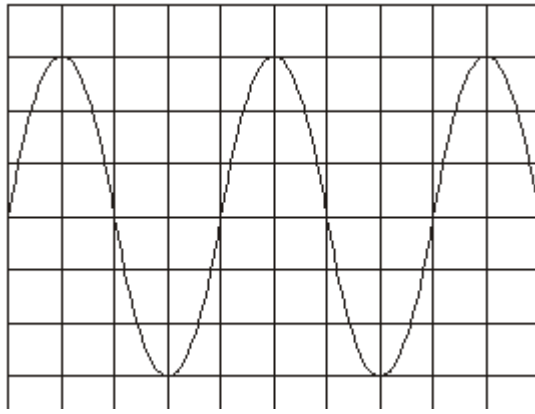

For the ac source, calculate

- (i) the frequency,

- (ii) the rms voltage.

(4)

- (b) The resistors have the following values: $R_1 = 450 \Omega$ and $R_2 = 90 \Omega$. Calculate

- (i) the rms current in the circuit,

- (ii) the rms voltage across R_2 .

(2)

- (c) Oscilloscope 2 is used to check the calculated value of the voltage across R_2 . The screen of oscilloscope 2 is identical to that of oscilloscope 1 and both are set to the same time base. Oscilloscope 2 has the following range for voltage sensitivity: 1 V per div., 5 V per div., 10 V per div. and 15 V per div. State which voltage sensitivity would give the most suitable trace. Explain the reasons for your choice.

(3)
(Total 9 marks)