

Name of the Student: \_\_\_\_\_

Max. Marks : 24 Marks

Time : 24 Minutes

Mark Schemes

**Q1.**

(a) (i) (use of  $G = -\frac{R_f}{R_a}$  gives)  $G = -\frac{300(k\Omega)}{30(k\Omega)}$  (1)  
 $= -10$  (1)

- (ii) waveform to be:  
 sinusoidal with same frequency as input waveform (1)  
 inverted with respect to input waveform (1)  
 peak value of  $\pm \approx 10$  V (1)  
 (allow C.E. for incorrect value of G from (i))

5

- (b) waveform to be:  
 clipped (1)  
 at  $\approx \pm 15$  V (1)

2

[7]

**Q2.**

(a) voltage at A =  $\frac{12 \times 8}{18}$  (1) = 5.3 V

voltage at B =  $\frac{12 \times 14}{18}$  = 9.3 V (1)

(3)

- (b) (i) for op-amp. 1,  $V_+ > V_-$  (1)  
 $\therefore$  output (saturated) at +12 V,  $\therefore$  P is lit (1)
- (ii) for op-amp. 2,  $V_- > V_+$  (1)  
 $\therefore$  output (saturated) at -12 V,  $\therefore$  Q is unlit (1)

(4)

(c) for P,  $V = IR$  gives  $12 - 1.6 = 20 \times 10^{-3} \times R$  (1)  
 $R = 520 \Omega$  (1)

(2)

[9]

**Q3.**


- (a) (i) negative feedback: part or all of the output is fed back to the input  
180° out of phase (1)

achieved through  $R_f$  (1)

- (ii) greater stability  
less distortion  
increased bandwidth  
gain predictable  
any two (1) (1)

4

(b)

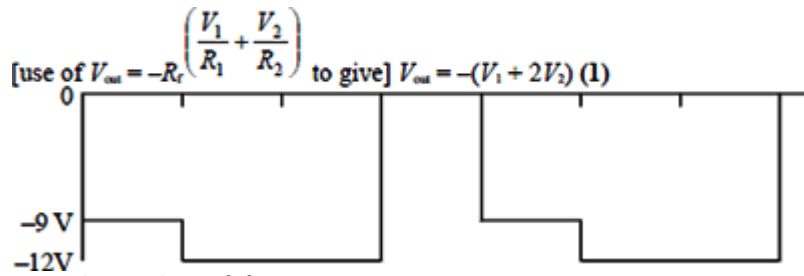

- negative values (1)  
correct 9 V and 12 V (1)  
saturation (1)  
repeated (1)

max 4

[8]