

Name of the Student: _____

Max. Marks : 22 Marks

Time : 22 Minutes

Mark Schemes

Q1.


- (a) range of frequencies in signal ✓
 reference to frequency at which signal drops by
 e.g. power 3dB (50%) / voltage 6dB (71%) ✓

2

- (b) low pass / treble cut ✓

1

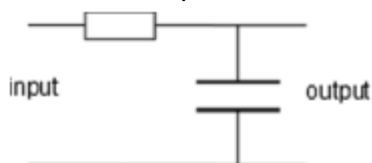- (c) (i) RC filter circuit, with input & output labelled ✓
 correct R & C positions ✓



2

- (ii) substitute values into $f = 1 / 2\pi RC$ ✓
 rearrange for C ✓
 40 (39.7) nF ✓

3

- (d) (i) gain > 1 ✓

1

- (ii) 100Hz ✓

1


- (iii) gain = 0.2 ✓ output = 0.4V ✓

2

[12]

Q2.

- (a)

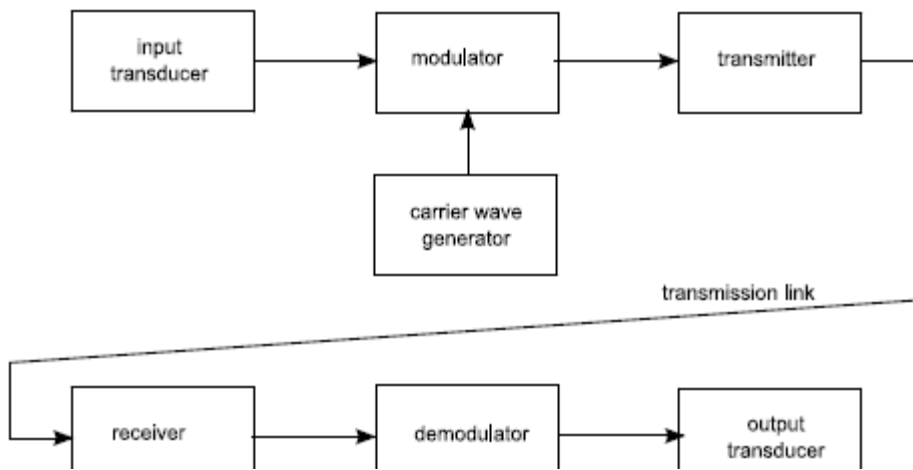

transmitter & receiver, carrier wave gen ✓
 demodulator & modulator ✓

2

- (b) e.g. free space
 optical fibre
 twisted pair
 coax cable (any 3 ✓✓✓)

3

- (c) (i) superimpose the information signal onto the carrier wave ✓

1

- (ii) AM – constant frequency sinusoidal wave matching carrier wave ✓
 amplitude varies in phase with information signal ✓
 FM – constant amplitude sinusoidal wave ✓
 frequency varies in phase with information signal ✓

4

[10]