

(c)	<p>Either refers to $W = Q^2/2C$ Or $W \propto Q^2$ (1) If Q halves, $W \rightarrow Q^2/8C$ Or halving Q quarters W (1) (Since W becomes a quarter in the time for Q to half) it takes less time for the energy to halve than the charge to halve. (dependent mark on either MP1 or MP2) (1)</p> <p>Or Refers to $W = QV/2$ (1) Q and V both decrease over time (1) W will decrease faster so takes less time to half in value. (dependent mark on either MP1 or MP2) (1)</p>	3
(d)	<p>Synchronous readings Or data logger records readings at exact time (1) Or voltmeter and stop watch need 2 people and data logger only one</p> <p>More readings can be taken in a shorter time Or higher sampling rate (1)</p> <p>(treat as neutral any reference to graph plotting automatically, human reaction time or accuracy)</p>	2
Total for question		12

Q2.

Question Number	Answer	Mark
(a)(i)	Capacitor, resistor, supply and switch all in series (ignore voltmeter) (1) Voltmeter directly across capacitor (1)	2
(a)(ii)	Datalogger allows large number of readings to be taken Or graph can be plotted directly/automatically Or simultaneous reading of t and V can be taken Or idea that people can't record quickly enough, (treat as neutral accuracy, precision misreading or human reaction time) (1)	1
(b)	Use of $C = Q/V$ (1) $Q = 5.0 \times 10^{-4} \text{ C}$ (1) <u>Example of calculation</u> $Q = 100 \times 10^{-6} \text{ F} \times 5.0 \text{ V}$ $Q = 5.0 \times 10^{-4} \text{ C}$	2

(c)(i)	Use of $I = \Delta Q / \Delta t$ e.c.f their value of C from (b) (1) $I = 0.05 \text{ A}$ (1) (accept recalculation of Q using $V = 4.90$ or 4.95 V) <u>Example of calculation</u> $I = 5.0 \times 10^{-4} \text{ C} / 10 \times 10^{-3} \text{ s}$ $I = 0.05 \text{ A}$	2
(c)(ii)	tangent drawn at $t = 0$ (1) $\Delta V / \Delta t = 2000 - 3300 \text{ V s}^{-1}$ (1) Initial current = $0.22 - 0.28 \text{ A}$ (1) (MP2 & 3 can be scored even if no tangent drawn) (No credit for exponential calculation) <u>Example of calculation</u> $\Delta V / \Delta t = 1.1 \text{ V} / 0.5 \text{ ms} = 2200 \text{ V s}^{-1}$ $I = (\Delta V / \Delta t) \times C$ $I = 2200 \text{ V s}^{-1} \times 100 \times 10^{-6} \text{ F}$ $I = 0.22 \text{ A}$	3
(c)(iii)	Use of $V = IR$ using answer from (ii) (1) correct evaluation of R (5 V used with current range in (ii) gives (1) $18 - 23 \Omega$) <u>Example of calculation</u> $5 \text{ V} = 0.22 \text{ A} \times R$ $R = 23 \Omega$	2
Total for question		12