

Question Number	Answer		Mark
(a)(i)	Use of $Q = CV$ $Q = 3900 \text{ (C)}$ <u>Example of answer</u> $Q = 1500 \text{ F} \times 2.6 \text{ V}$ $Q = 3900 \text{ C}$	(1) (1)	2
(a)(ii)	Straight line through the origin Passing through 2.6 V and answer to (a)(i) or 4000 C	(1) (1)	2
(a)(iii)	Use of $W = QV/2$ Or $W = CV^2/2$ Or use of area under graph $W = 5.1 \text{ kJ}$ (use of 4000 C gives $W = 5.2 \text{ kJ}$ (allow ecf from (a)(i))) <u>Example of answer</u> $W = 3900 \text{ C} \times 2.6 \text{ V} / 2$ $W = 5070 \text{ J}$	(1) (1)	2
(b)(i)	Exponential decay Current decreases by equal fractions in equal time intervals	(1) (1)	2
(b)(ii)	See attempt of I_0/e Finds time (accept 0.75-0.80s) Use of $\tau = RC$ $R = 0.0005 \Omega$ Or Finds the time for I_0 to half Uses $t_{1/2} = \tau \ln 2$ Use of $\tau = RC$ $R = 0.00050 - 0.00053 \Omega$ Or	(1) (1) (1) (1) (1) (1) (1) (1)	

	<p>See attempt of 37% of 5400 A (1)</p> <p>Finds time (accept 0.75 to 0.80 s) (1)</p> <p>Use of $\tau = RC$ $R = 0.0005 - 0.00053\Omega$ (1)</p> <p>Or (1)</p> <p>Draws tangent at $t = 0$ to meet time axis.</p> <p>Records intercept of tangent with axis (accept 0.6 s - 0.9 s) (1)</p> <p>Use of $\tau = RC$ (1)</p> <p>$R = 0.0004 \Omega - 0.0006 \Omega$ (1)</p> <p>Or (1)</p> <p>reads a value off the y-axis and corresponding time</p> <p>Subs into formula using 5400 (A) to find RC (1)</p> <p>Substitutes for C to find R (1)</p> <p>$R = 0.00050 \Omega - 0.00058 \Omega$ (1)</p> <p>(1)</p> <p><u>Example of calculation</u></p> <p>37% of 5400 A is 1998 A (1)</p> <p>Time to fall to this value is 0.75 s (1)</p> <p>$RC = 0.75$ s (1)</p> <p>$R = 0.75$ s / 1500 F = 0.0005 Ω (1)</p>	4
(c)	<p>Max 3</p> <p>Ultracapacitor used for:</p> <p>overtaking Or going up a hill Or starting (from rest) Or accelerating. (1)</p> <p>Because this requires a large <u>current/power</u>. (1)</p> <p>Batteries used for travelling at constant speed (1)</p> <p>Because this requires a small <u>current/power</u> for a longer time (1)</p>	3
	Total for question	15