

Name of the Student: _____

Max. Marks : 25 Marks

Time : 25 Minutes

Mark Schemes

Q1.

(a)



1

(b) charge

1

(c) place the component / thermistor in the water / beaker

1

record the temperature (of the water) using the thermometer
*allow place the thermometer in the water / beaker and
record the temperature*

1

record / measure the resistance (using the resistance meter)

1

change the temperature of the water (using the kettle) and repeat the measurements (of
temperature and resistance)

1

(d) non-linear

1

(e) (resistance changes from) 200 (Ω) to 80 (Ω)

1

change in resistance = 120 (Ω)

1

(f) power = potential difference \times current

or

$$P = VI$$

1

(g) 2900 = 230 \times I

1

$$I = \frac{2900}{230}$$

1

$$I = 12.6... \text{ (A)}$$

allow 13 (A)

1

[13]

Q2.

(a) battery

1

(b) variable resistor

allow resistor

allow battery / cells

allow correct circuit symbol

1

(c) subtract 0.4 volts from each reading

1

(d) mean = $\frac{0.54+0.58+0.53}{3}$

1

allow mean = $\frac{1.65}{3}$

mean = 0.55 (A)

1

(e) $P = 4.8 \times 0.75$

1

$P = 3.6 \text{ (W)}$

1

(f) $R = \frac{4.8}{0.75}$

1

$R = 6.4 \text{ (}\Omega\text{)}$

1


(g) increase

1

increase

1

(h)

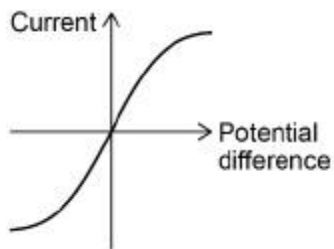

1

[12]