


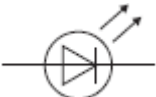
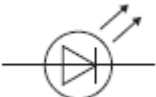
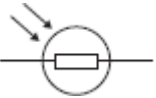
Name of the Student: \_\_\_\_\_

Max. Marks : 19 Marks

Time : 19 Minutes

**Q1.**

(a) Draw **one** line from each circuit symbol to its correct name.

Circuit symbol	Name
	Diode
	Light-dependent resistor (LDR)
	Lamp
	Light-emitting diode (LED)

(3)

(b) **Figure 1** shows three circuits.

The resistors in the circuits are identical.


Each of the cells has a potential difference of 1.5 volts.

**Figure 1**

**Circuit 1**

**Circuit 2**

**Circuit 3**

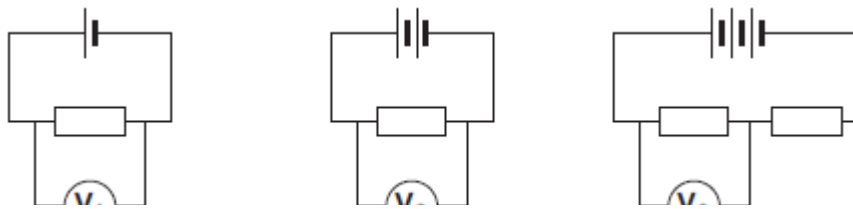

(i) Use the correct answer from the box to complete the sentence.

**half                  twice                  the same as**

The resistance of **circuit 1** is \_\_\_\_\_ the resistance of **circuit 3**.

(1)

(ii) Calculate the reading on voltmeter  $V_2$ .

\_\_\_\_\_

Voltmeter reading  $V_2 =$  \_\_\_\_\_ V

(1)

(iii) Which voltmeter,  $V_1$ ,  $V_2$  or  $V_3$ , will give the lowest reading?

Draw a ring around the correct answer.

$V_1$

$V_2$


$V_3$

(1)

(c) A student wanted to find out how the number of resistors affects the current in a series circuit.

**Figure 2** shows the circuit used by the student.

**Figure 2**

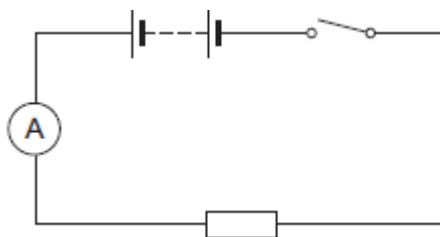


The student started with one resistor and then added more identical resistors to the circuit.

Each time a resistor was added, the student closed the switch and took the ammeter reading.

The student used a total of 4 resistors.

**Figure 3** shows three of the results obtained by the student.

**Figure 3**

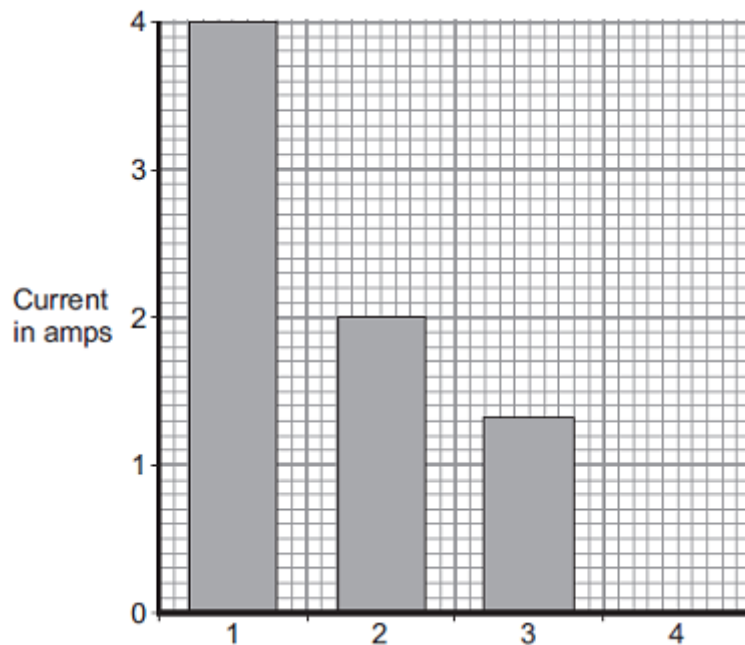

- (i) To get valid results, the student kept one variable the same throughout the experiment. Which variable did the student keep the same?

---

(1)

- (ii) The bar chart in **Figure 3** is not complete. The result using 4 resistors is not shown. Complete the bar chart to show the current in the circuit when 4 resistors were used.

(2)

- (iii) What conclusion should the student make from the bar chart?

---



---

(1)



(Total 10 marks)

## Q2.

- (a) **Figure 1** shows the inside of a three-pin plug and a length of three-core cable.

The cable is to be connected to the plug.

**Figure 1**

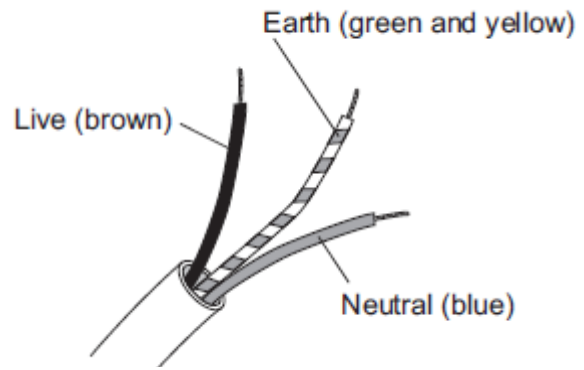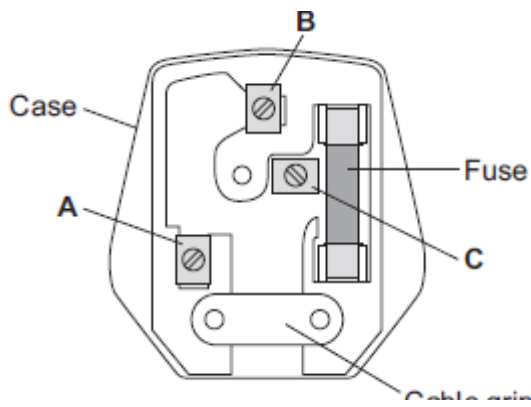

- (i) Complete **Table 1** to show which plug terminal, **A**, **B** or **C**, connects to each of the wires inside the cable.

**Table 1**

Wire	Plug terminal
Live	
Neutral	
Earth	

(2)


- (ii) Name a material that could be used to make the case of the plug.

\_\_\_\_\_


(1)

- (b) **Figure 2** shows an electric drill and an extension lead. The drill is used with the extension lead.

**Figure 2**

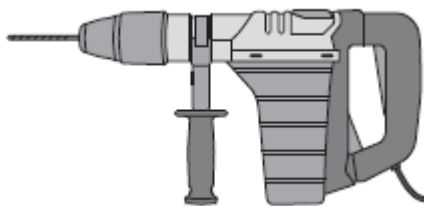

Electric drill

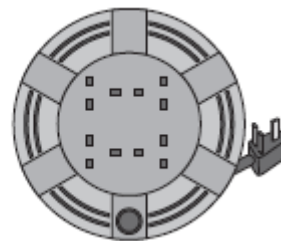

Extension lead

- (i) The drill is used for 50 seconds.

In this time, 30 000 joules of energy are transferred from the mains electricity supply to the drill.

Calculate the power of the drill.

\_\_\_\_\_  
\_\_\_\_\_

Power = \_\_\_\_\_ W

(2)

(ii) A second drill is used with the extension lead. The power of this drill is 1200 W.

The instructions for using the extension lead include the following information.

**When in use the lead may get hot:**

**DO NOT go over the maximum power**

- lead wound inside the case: 820 watts
- lead fully unwound outside the case: 3100 watts

It would **not** be safe to use this drill with the extension lead if the lead was left wound inside the plastic case.

Explain why.

---

---

---

---

---

---

---

(3)

(c) **Table 2** gives information about three different electric drills.

**Table 2**

Drill	Power input in watts	Power output in watts
X	640	500
Y	710	500
Z	800	500

A person is going to buy **one** of the drills, **X**, **Y** or **Z**. The drills cost the same to buy.

Use only the information in the table to decide which **one** of the drills, **X**, **Y** or **Z**, the person should buy.

Write your answer in the box.

Give a reason for your answer.

---

---

---

(1)  
(Total 9 marks)