

Name of the Student: _____

Max. Marks : 21 Marks

Time : 21 Minutes

Mark Schemes

Q1.

(a) the polarity (of the supply) does not change
allow potential difference in one direction (only) 1

(b) energy transferred = power × time 1

(c) 162 000 000 = 7200 × t 1

$$t = \frac{162\,000\,000}{7200} \quad 1$$

$$t = 22\,500 \text{ (s)} \quad 1$$

(d) $V = I \times R$ 1

(e) 480 = 15 × R 1

$$R = \frac{480}{15} \quad 1$$

$$R = 32 \text{ (}\Omega\text{)} \quad 1$$

(f) time taken using system **A** is double the time of system **B** 1

[10]**Q2.**

(a) ammeter and voltmeter symbols correct 1

voltmeter in parallel with lamp 1

ammeter in series with lamp 1


- (b) smooth curved line of correct shape
do not accept a line that becomes horizontal

1

passing through - 4.0 V, - 0.2 A

or

- 6.0 V, - 0.23 A

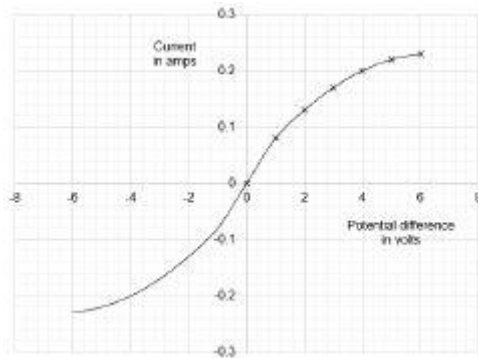

2nd mark conditional on scoring 1st mark

1

- (c) potential difference = current × resistance

or

$$V = IR$$

1

- (d) $I = 0.08$ (A)

1

$$1.0 = 0.08 \times R$$

allow $1.0 = \text{their } I \times R$ provided their I has been obtained from the graph

1

$$R = \frac{1.0}{0.08}$$

allow $R = \frac{1.0}{\text{their } I}$

1

$$R = 12.5 \text{ } (\Omega)$$

allow an answer consistent with their I

1

- (e) ammeter displays a reading when not connected (to a circuit)

1

[11]