

Name of the Student: _____

Max. Marks : 18 Marks

Time : 18 Minutes


Mark Schemes

Q1.

(a) 800 (W)

accept 0.8kW but this answer must have the unit

1

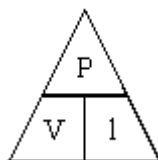(b) (i) power = voltage \times current*accept the equation rearranged**accept $P = VI$* *do not accept C for current**do not accept $P = VA$* *do not accept power = VA**do not accept**unless subsequent calculation shows understanding*

1

(ii) 3.5 (A)

*accept a larger number of d.p. but you must be able to round to 3.5**allow 1 mark for*

$$\text{current} = \frac{\text{power}}{\text{voltage}}$$

$$\text{or } (I =) \frac{800}{230}$$

2

(iii) 5 (A)

independent of (ii) unless e.c.f from part (b)(ii)

1

(c) 0.95 or 95 (%)

allow 1 mark if useful energy output is given as 760 ignore any incorrect unit

2

[7]

Q2.

(a) C

award mark if A and B identified as not filament lamp

1

resistance increases

negated by wrong statement e.g. current goes down

1

as the lamp gets hot

*accept as current (through lamp) **or** voltage (across lamp) increases
do **not** accept non-ohmic reason independent of choice of component*

1

(b) ammeter wire and battery only in series

*non standard symbols acceptable if correctly identified (labelled) for
ammeter, voltmeter and battery*

1

voltmeter only in parallel with wire **or** battery

*all in series **or** ammeter in parallel neither of these two marks awarded*

1

all symbols correct

ignore lines drawn through centres of symbols


1

(c) (i) voltage = current \times resistance

accept $V = I \times R$

accept volts = amps \times ohms

*do **not** accept $V = C \times R$*

accept 

if subsequent method correct

1

(ii) 30

accept correct substitution for 1 mark (9/0.3)

2

ohms

accept correct symbol Ω

1

(iii) goes up

must be a comparison

accept calculation if answer is larger than c (ii)

1

[11]