


Name of the Student: \_\_\_\_\_

Max. Marks : 19 Marks

Time : 19 Minutes

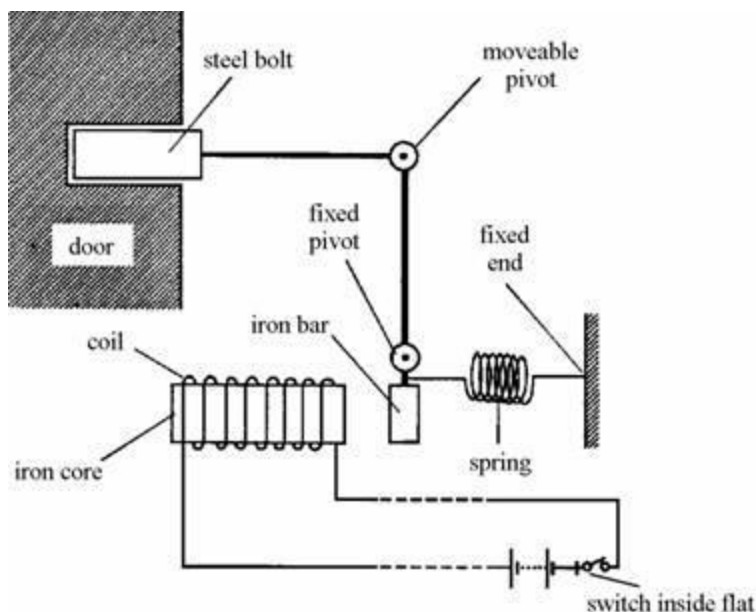**Q1.**

The diagram below shows a door lock which can be opened from a flat inside a building.



(a) Explain how the door is unlocked when the switch is closed.

---

---

---

---

(4)

(b) State **two** changes which would increase the strength of the electromagnet.

1. \_\_\_\_\_

2. \_\_\_\_\_

(2)

(c) Why is the spring needed in the lock?

---

---

(1)


(d) The connections to the coil were accidentally reversed. Would the lock still work?

Explain your answer.

(2)  
(Total 9 marks)

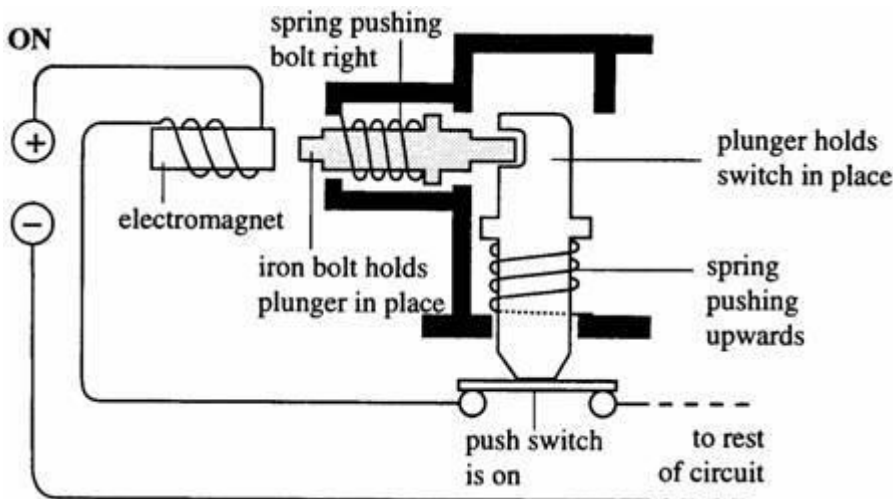**Q2.**

A fault in an electrical circuit can cause too great a current to flow. Some circuits are switched off by a circuit breaker.



One type of circuit breaker is shown above. A normal current is flowing. Explain, in full detail, what happens when a current which is bigger than normal flows.

---

---

---

---

---

---

---

---


---

---

(Total 4 marks)

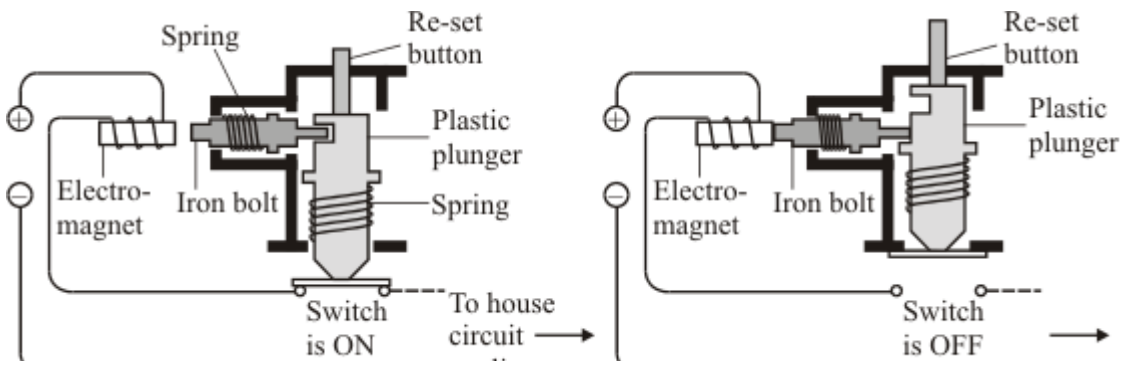**Q3.**

Circuit breakers help to make the electricity supply in homes safer. A circuit breaker is an automatic safety switch. It cuts off the current if it gets too big.



Describe, in as much detail as you can, how this circuit breaker works.

*To gain full marks in this question you should write your ideas in good English. Put them into a sensible order and use the correct scientific words.*

---



---



---



---



---



---



---



---



---



---



---



---



---



---



---



---



---



---



---



---



---



---

**(Total 6 marks)**