

Name of the Student: _____

Max. Marks : 19 Marks

Time : 19 Minutes

Mark Schemes

Q1.

Question number	Answer	Mark
(a)	B	(1)
Question number	Answer	Mark
(b)	substitution into correct equation (1) $= 1.9 \times 10.0 \times 9.0$ answer (1) 171 (J) (which is about 170 J) Answer must be shown to 3 significant figures	(2)
Question number	Answer	Mark
(c)	B	(1)
Question number	Answer	Mark
(d)	An explanation that combines identification – understanding (1 mark) and reasoning/justification – understanding (2 marks): <ul style="list-style-type: none"> • the coil contains wires which have a resistance (1) • and current in the wire is due to movement of electrons through (close-packed) lattice of positive ions (1) • hence collisions between electrons and ions in the lattice transfer energy from electrons to the lattice (causing the temperature of the wires/coil to rise) (1) 	(3)


		Indicative Content	Mark
		<p>A explanation including some of the following points</p> <p>Light dependent resistors (LDR)</p> <ul style="list-style-type: none"> • Resistance changes with light intensity • Bright light , low resistance • No light (dark), high resistance • Low resistance gives high current.(RA) <p>Thermistor</p> <ul style="list-style-type: none"> • Resistance changes with temperature • Negative temperature coefficient • High temperature, low resistance • Low temperature, high resistance • Low resistance gives high current (RA) 	(6)
Level	0	No rewardable content	
1	1 - 2	<ul style="list-style-type: none"> • a limited explanation linking light affecting LDR AND heat affecting thermistor OR a correct relationship for one device, e.g. thermistors change resistance when the temperature changes and LDRs change resistance when it gets dark OR the resistance decreases/ current increases of a LDR when the light gets brighter • the answer communicates ideas using simple language and uses limited scientific terminology • spelling, punctuation and grammar are used with limited accuracy 	
2	3 - 4	<ul style="list-style-type: none"> • a simple explanation correctly linking the temperature and light with resistance or current for both devices OR a correct relationship for one device with a link to the way this affects the current and resistance. 	

		<p>e.g. the resistance of a LDR increases when the light gets dimmer and when the temperature lowers the resistance of a thermistor increases OR the resistance of a LDR decreases when the light gets brighter and this increases the current</p> <ul style="list-style-type: none"> the answer communicates ideas showing some evidence of clarity and organisation and uses scientific terminology appropriately spelling, punctuation and grammar are used with some accuracy
3	5 - 6	<ul style="list-style-type: none"> a detailed explanation including the qualitative relationships for both devices and a link to the way resistance change affects the current in BOTH of them, e.g. the resistance of a LDR is less when the light gets brighter which increases the current. When the temperature lowers the resistance of a thermistor increases. This means that the current will decrease as the thermistor cools down. the answer communicates ideas clearly and coherently uses a range of scientific terminology accurately spelling, punctuation and grammar are used with few errors

Q3.

	Answer	Acceptable answers	Mark
	<p>A suggestion to include any 2 of the following</p> <ul style="list-style-type: none"> (LED) turns on and off as voltage/current changes direction/from +ve to -ve/ twice each second (1) (LED) on for (+ve) part of cycle (1) (LED) off for (-ve) part of cycle (1) 	<p>Flash(es) / flicker(s) (on and off) current changes every 0.25 s /4 times each second Turns on twice each second = 2 marks Only on when voltage/current is +ve gains both marks</p>	(2)

Q4.

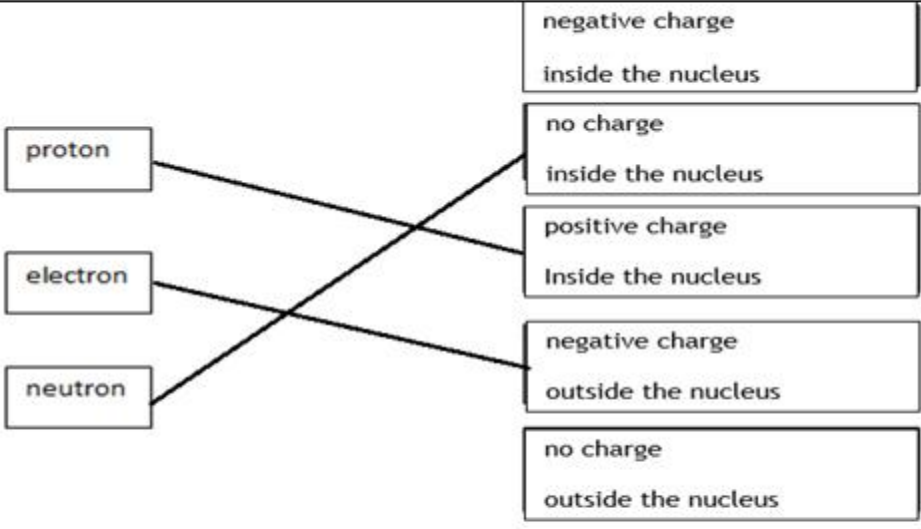Question Number	Answer	Mark
	 <p data-bbox="327 728 829 761">One mark for each correct line.</p> <p data-bbox="327 817 1300 884">More than one line from a box on the left loses the mark for that box.</p>	(3)