

Name of the Student: _____

Max. Marks : 22 Marks

Time : 22 Minutes

Mark Schemes

Q1.

Question number	Answer	Additional guidance	Mark
(i)	recall and substitution (1) $V = 0.20 \times 15$ evaluation (1) 3 (V)	7(V) gains 1 mark (use of $15 + 20$) award full marks for the correct answer without working	(2)

Question number	Answer	Additional guidance	Mark
(ii)	addition and substitution (1) (P=) $0.20^2 \times 35$ evaluation (1) 1.4 (W)	award full marks for the correct answer without working	(2)

Question Number	Answer	Additional guidance	Mark
(i)	<p>recall and substitution into $P = I^2 \times R$ (1)</p> <p>$130 = 14^2 \times R$</p> <p>rearrangement (1)</p> $R = \frac{130}{14^2}$ <p>evaluation to 2 sig fig (1)</p> <p>$(R =) = 0.66 \text{ } (\Omega)$</p>	<p>substitution and rearrangement may be in either order</p> <p>alternative route:</p> $V \left(= \frac{P}{I} \right) = \frac{130}{14} \text{ OR } 9.3 \text{ V}$ <p>(1)</p> $R \left(= \frac{V}{I} \right) = \frac{9.3}{14}$ <p>(1)</p> <p>award full marks for the correct answer without working</p> <p>award 2 marks for 0.663.. or 0.67</p>	(3)

Question Number	Answer	Additional guidance	Mark
(ii)	<p>rate of flow of charge in the immersion heater is greater than in the kettle / heating element (1)</p> <p>the direction of the flow of charge in the kettle / heating element keeps changing (whereas it remains in the same direction in the immersion heater) (1)</p>	<p>accept reverse arguments</p> <p>more charge per second in the immersion heater</p> <p>allow (in this context) faster (rate of) flow in immersion heater</p> <p>14 coulombs per sec in immersion heater and 8.3 coulombs per sec in kettle / heating element</p> <p>flows both ways in the kettle / heating element (one way in the heater)</p> <p>simply referring to alternating current and direct current is not enough</p>	(2)

Q3.

Question number	Answer	Additional guidance	Mark
(i)	Substitution and evaluation (1) 15 (Ω)		(1) AO2.1

Question number	Answer	Additional guidance	Mark
(ii)	select / recall (1) (power =) $V \times I$ or (power =) $I^2 \times R$ or (power =) $\frac{V^2}{R}$ substitution and evaluation (1) (power =) 1.4 (W)	 (power =) 4.5×0.3 $0.3^2 \times 15$ $\frac{4.5^2}{15}$ allow 1.3(5) (W) award full marks for the correct answer without working	(2) AO2.2

Q4.

Question number	Answer	Additional guidance	Mark
	<p>substitution (1)</p> <p>$1.56 = 0.45 \times R$</p> <p>rearrangement and evaluation (1)</p> <p>(R =) 3.5 (ohms)</p>	<p>alternative method rearrangement (1)</p> <p>(R =) $\frac{V}{I}$</p> <p>or</p> <p>(R=) $\frac{1.56}{0.45}$</p> <p>(substitution and) evaluation (1)</p> <p>(R =) 3.5 (ohms)</p> <p>allow values that round to 3.5 e.g. 3.46(666) 3.47 etc</p> <p>award full marks for the correct answer without working</p>	<p>(2) AO2</p>

Q5.

Question Number	Answer	Additional guidance	Mark
(i)	<p>recall and substitution into $V = IR$ (1) $5.0 = 0.26 \times R$</p> <p>rearrangement (1) $(R =) \frac{5.0}{0.26}$</p> <p>evaluation (1) $19 (\Omega)$</p>	<p>accept substitution and rearrangement in either order</p> <p>$(R =) \frac{V}{I}$</p> <p>$\frac{5.0}{0.26}$ scores 2 marks</p> <p>accept answers that round to $19 (\Omega)$ (e.g. 19.23)</p> <p>accept answer written table if not written on answer line.</p> <p>award full marks for the correct answer without working</p>	(3)

Question Number	Answer	Additional guidance	Mark
(ii)	<p>a comment that includes the following points</p> <p>idea that resistance increases with potential difference (1)</p> <p>idea that doubling the potential difference does not result in doubling of resistance (1)</p> <p>OR</p> <p>$V = \text{constant} \times R$ is not supported by this data (1)</p> <p>correct processing of data from the table to support either of the above mark points (1)</p>	<p>idea that equal increments of potential difference do not cause equal increments of resistance</p> <p>reverse argument e.g. if student was correct then equal increments of p.d. would cause equal increment of resistance</p> <p>if student was correct then current would be constant</p> <p>ignore simple quoting of data for this mark</p>	(3)

Question Number	Answer	Additional guidance	Mark
(iii)	<p>A description that includes</p> <p>add a variable resistor (1)</p> <p>with</p> <p>in series (with the lamp / power supply) (1)</p> <p>OR</p> <p>add a potential divider (1)</p> <p>with</p> <p>in parallel with power supply (1)</p>	<p>marks may be obtained from a circuit diagram</p> <p>rheostat</p> <p>accept between / before / after for in series</p> <p>potentiometer</p> <p>across the power supply</p> <p>ignore replacing power supply / using fixed resistor(s) / LDR / thermistor</p> <p>in both cases, second mark conditional on first mark</p>	(2)