

Name of the Student: _____

Max. Marks : 24 Marks

Time : 24 Minutes

Mark Schemes

Q1.

- (a) Amount of **chemical energy** transferred / converted to **electrical energy** for 1 C of charge (through the battery).

ORWork done in moving 1 C of charge **whole way** round circuit ✓*Allow:**(The emf is) the terminal pd (of the battery) when there is no current in the battery.*

1

- (b) Use of $Q = It$

OR*Substitutes for I and t .**($Q =$) $0.044 \times 37 \times 60$ **OR****($Q =$) 0.044×2220 **OR****($Q =$) 97.68 (C)*Use of $Q = Ne$ ✓*($N =$) $\frac{\text{their } Q}{1.6 \times 10^{-19}}$ or ($N =$) $6.25 \times 10^{18} \times \text{their } Q$* *their Q must have supporting work which identifies it as Q* *($N =$) 6.1×10^{20} ✓**Accept answer correctly rounded to at least 2 sf.**Calculator display = 6.105×10^{20}*

2

- (c) Read off $V = 3.4$ V when $I = 44$ (mA) ✓

Accept any of the following pairs of values:

I (mA)	V (V)	P (W)
4 to 6	2.8	0.011 to 0.017
8 to 12	2.9	0.023 to 0.035
12 to 15	3	0.036 to 0.045
20	3.1	0.062
22 to 26	3.2	0.070 to

		0.083
40 to 47	3.4	0.136 to 0.160
64 to 72	3.6	0.23 to 0.26
96 to 100	3.8	0.36 to 0.38

Use of $P = VI$ ✓

Substitutes a voltage between 2.8 V and 3.8 V and a corresponding current value from table. Expect to see a consistent power in range quoted for that voltage.

Condone POT error in sub for current and its subsequent power. In MP1 and MP2

OR Uses $I = 0.044$ (A) and $3\text{ V} < V < 4\text{ V}$ and obtaining a consistent answer.

($P =$) 0.15 (W) ✓

Accept answer correctly rounded to at least 2 sf.

MP3 must be 0.15 (W) or 0.150 (W) or 0.1496 (W).

3

(d) **MP1** ✓

Use of $V = IR$: (to find lost volts = $Ir =$) 0.044×1.5 OR 0.066 V

OR

$$\left(\frac{\varepsilon}{I} =\right) \frac{12}{0.044} \text{ (To find total resistance = } \frac{3000}{11} \text{ or } 272.7\text{ }(\Omega))$$

MP2 ✓

$$\text{(Total resistance - } r = R =) \frac{5967}{22} \text{ or } 271.2\text{ }(\Omega)$$

OR

$$\text{(Pd across } R =) 271.2 \times 0.044 \text{ or } 11.9328\text{ V or their } R \times 0.044$$

OR

$$\text{(Total pd across LEDs =)} 3 \times 3.4 \text{ or } 10.2\text{ V} \quad \text{ECF}$$

OR

$$\text{(Resistance of an LED =)} \frac{3.4}{0.044} \text{ or } 77.3\text{ }(\Omega) \quad \text{ECF}$$

OR

$$\text{(Resistance of an LED = } \frac{P}{I^2} =) \frac{0.15}{0.044^2} \text{ or } 77.3 \text{ or } 77.48\text{ }(\Omega) \quad \text{ECF}$$

MP3 ✓

(Total resistance of 3 LEDs =) 3×77.3 or 231.9 or 232.438 (Ω) or 3 x their resistance of one LED

OR

(Pd across **R** =) 12 - their total pd across LED - their lost volts or 1.734 (V)

OR

$R = R - 3 \times$ their resistance of one LED

OR

(R of **R** =) $\frac{\text{their pd across unknown resistor}}{0.044}$ or $\frac{1.734}{0.044}$

MP4✓

(R of **R** =) 39(.4) (Ω) or 38.8 (Ω)

Alternative

MP1 Use of $\varepsilon = I(R + r)$ by substituting
for ε , I and r (where R is external resistance)

MP2

Rearrange $\varepsilon = I(R + r)$ to find $R = 271.2 (\Omega)$

Condone POT in any of the working for **MP1**, **MP2** and **MP3**.

Condone answers in range 38.5 Ω to 39.7 Ω

Treat use of their V from (c) as an ECF e.g.

An answer of 53 (Ω) gains **4 marks** (uses $V = 3.2$ V)

Other consistent uses of their V identifiable in (c) can achieve **4 marks**.

4

(e) **MP1**

lost volts = 3.5×1.5 or 5.25 V

OR

Current in LEDs = 8 mA (when $V = 2.9$ V)

Allow between 8 mA and 10 mA for this read-off.

OR

LEDs require 8.7 V to light✓

MP2

terminal pd = 6.75 V✓

MP3

LEDs won't light:

-because terminal pd is less than 8.7 V

-because pd across LED is less than 2.5 V, therefore, no current in LEDs

-because pd across **R** is zero as the resistance of LED is much greater than **R**, therefore, no current in LEDs

-Resistor **R** would require a pd of 0.315 V. Therefore, total pd required = 9.01 V is greater than terminal pd.

-their pd across each LED is below switch-on voltage (of 2.9 V)✓

MP3 gives a valid reason why 6.75 V is insufficient.

Needs to state LEDS won't light for to gain MP3.

3

[13]

Q2.

- (a) (1 C of) the charge gains ϵ J on passing through cell

OR

energy transferred (by 1 C) in R_1 is V_1 (J)

OR

energy transferred (by 1 C) in R_2 is V_2 (J)

OR

energy transferred (by 1 C) in r is Ir (J) ✓

If no other mark awarded, allow one mark for definition of emf in terms of energy transfer.

accept: 'dissipated'

accept 'lost volts' for Ir but reject 'voltage across r '

accept 'work done' for 'energy transferred'

(for conservation of energy)

$$\epsilon = IR_1 + IR_2 + Ir \quad \checkmark$$

Alternative for MP2

$$\epsilon = V_1 + V_2 + Ir$$

provided that MP1 is awarded.

2

- (b) Equates emf to $Ir + 2.89$ in some form ✓₁

If no other mark awarded, award one mark for use of emf value in MP2.

Allow in MP1 (their current/A) $\times 125\Omega$ for 2.89 V

Calculates I from $2.89 \div 125 (=0.02312 \text{ A})$ ✓₂

Allow alternative routes for ✓₁ and ✓₂. E.g.

$$\text{'Lost volts'} = 0.11 \text{ V} \quad \checkmark_1$$

Applies potential-divider equation e.g.

$$0.11 \div 2.89 = r \div 125 \quad \checkmark_2$$

OR

$$3 \div (125 + r) = 2.89 \div 125 \quad \checkmark_1 \checkmark_2$$

Giving $r = 4.76 (\Omega)$ ✓₃

Must see at least 3 sf answer

Answer must round to 4.76(Ω)

- (c) (Resistance splits 25 Ω and 104.8 Ω)

Applies potential divider formula eg $\frac{V}{3.00} = \frac{25}{129.8}$ ✓

$V = 0.58$ (V) ✓

Accept other routes for MP1 e.g.

using $V = IR$, with 25 Ω and their current, for example from

• $I = 0.023$ A (from Q03.2)

• $I = \frac{\text{emf}}{\text{total resistance}} = \frac{3}{125 + r}$

• $I = \frac{\text{terminal pd}}{125}$

OR

using $V = \frac{2.89}{5}$ with an identification of 2.89 V as the terminal pd.

If no other mark awarded, allow one mark for using 29.8 Ω instead of 129.8 Ω for total resistance giving 2.5(2) V.

2

- (d) Any **four** from:


Straight line 0 V **A** to **P** ₁ ✓

Less steep non-zero gradient from **P** to **Q** ₂ ✓

Short steep increase at **Q** ₃ ✓

Q to **R** about same non-zero gradient as **P** to **Q** ₄ ✓

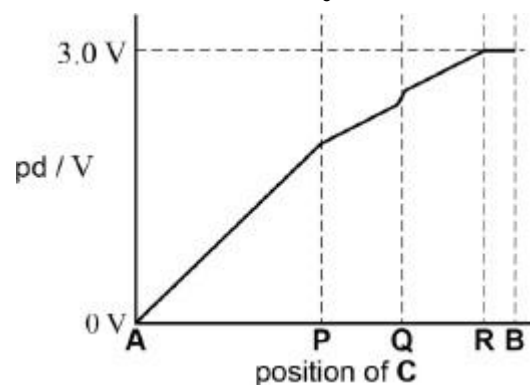Horizontal line from **R** to **B** at 3.0 V ₅ ✓



For ₃ ✓ allow range no greater than width of "Q" label on horizontal axis.

If graph sketched from 3 V (at **A**) to 0 V (at **B**) award **max 2** (based on ₂ ✓ and ₄ ✓).

If a single diagonal straight line from 0 V (at **A**) to **B**, award ₁ ✓ only.

If a single diagonal straight line from 0 V (at **A**) to **R** and then horizontal to **B**, award only ₁ ✓ and ₅ ✓ if scored (**ie max 2**).

Max 4

[11]