

Name of the Student: _____

Max. Marks : 24 Marks

Time : 24 Minutes

Mark Schemes

Q1.

- (a) Work done in moving 1 C of charge through the cell ✓
1.5 J of work is done in moving 1 C of charge through the cell ✓

OR

Amount of energy converted from other forms to electrical energy per 1 C of charge ✓

1.5 J of energy converted from other forms to electrical energy per unit charge (passing across the emf) ✓

OR

Work done in moving 1 C of charge (whole way) round circuit ✓

1.5 J of work is done in moving 1 C of charge the (whole way) round circuit ✓

2nd marking point obtains both marks

Max 1 mark available for the following:

The emf is the terminal pd when there is no current in the cell (and this equals 1.5 V)

1.5 J of energy per 1 C of charge.

Allow a statement of Kirchhoff's 2nd law for 1 mark. Where the law is in symbol form, the meaning of the symbols must be stated. Need a clear communication of internal and external resistances.

2

- (b) $P = VI$

And

$(P) = 0.465 \text{ (W)}$ ✓

Seen to more than 2 sf with supporting equation with subject seen in working

1

- (c) Use of appropriate power equation to determine wasted power
or
power dissipated in $R = \text{total power} - \text{their wasted power}$ ✓

$(P) = 0.40 \text{ W}$ ✓

Alternative for 1 mark:

Use of $I = \frac{\epsilon}{R+r}$

Or

$$pd \text{ across } R = 1.5 - 0.65 \times 0.31$$

or

$$pd \text{ across } R = 1.2985 \text{ (V)}$$

or

$$\text{total resistance} = 1.5 / 0.31$$

or

$$\text{total resistance} = 4.839 \text{ (}\Omega\text{)}$$

$$\text{or } R = 4.2 \text{ (}\Omega\text{)}$$

$$\text{or } P = I^2 \times \text{their } R$$

or

$$P = \frac{V^2}{R} \text{ using their } V \text{ and } R \checkmark$$

2

(d) Use of $E = P t$

$$\text{or } E = VI t$$

Or

$$E = QV \text{ and } Q = It \checkmark$$

Allow use of the equation with their values.

An answer of 3.5×10^4 is worth 1 mark

$$(t =) 3.0(1) \times 10^4 \text{ (s)} \checkmark$$

2

(e) **MAX 3 from (1 to 4) or (5 to 8)**

It is suitable, because:

(1) Current required in lamp = 0.62 A or use of $I = \frac{P}{V}$ seen

(2) Resistance of lamp = 2.11 Ω or use of $R = \frac{V^2}{P}$ seen \checkmark

(3) current in each cell = 0.31 A \checkmark

(4) lost volts = 0.2 V

or

$$\text{lost volts} = 0.65 \times 0.31 \checkmark$$

Check the diagram in part (e)

*Must have the **correct conclusion to award 4 marks.***

Conclusion: yes, terminal pd = **1.5 – 0.2** seen

or

$$\text{terminal pd} = 1.5 - 0.65 \times 0.4 / 1.3 \checkmark$$

OR

(5) total internal resistance = 0.325 Ω \checkmark

(6) total resistance in circuit = 2.44 Ω \checkmark

(7) Resistance of lamp = 2.11 Ω \checkmark

(8) pd splits in ratio of 0.325:2.11 \checkmark

Conclusion: yes, pd across lamp is $\frac{2.11 \times 1.5}{2.44}$ **(= 1.3 V) seen \checkmark**

Allow max 3 from a combination of two route [(2) and (7) worth total of 1 mark]

4

- (e) (Cells must be added) in parallel ✓

Because:

more energy stored in the bank of cells / less power from each cell ✓

without increasing the voltage across the bulb (above 1.5 V)

or

without increasing the terminal pd (above 1.5V) ✓

Must link the cells being added in parallel to one or both reason to gain three marks.

Alternative:

- *In parallel*
- *Current shared by cells*
- *Takes longer to convert the energy stored in each cell.*

Alternative:

- *In parallel*
- *Less internal resistance*
- *Less power / energy wasted*

Cells in series statement means no marks can be obtained.

3

[14]

Q2.

- (a) to limit (maximum) current (when variable resistor is set to zero) ✓

Accept 'so cell is not short-circuited' for 1 ✓

to prevent overheating (of cell)

OR

to prevent damage to cell

OR

otherwise cell would discharge quickly ✓

'to avoid damaging components' is not enough for 2 ✓

2

- (b) Line ruled through bottom of second error bar and top of ninth (3rd from right) error bar ✓

Ignore unit if given. Allow tolerance of 2 mm inside either error bar.

Determines their gradient, with $\Delta x \geq 0.2$ (A) ✓

$(-1.0 \pm 0.1) \text{ (V A}^{-1}\text{)}$ ✓

Expect to see 2 sf in any answer

3

- (c) Attempt to calculate mean of their G_{\min} and -1.3 ✓

Allow positive G values

1.1 (Ω) ✓

Ecf from (b). 1 mark max if r given as negative

2

- (d) States that $\varepsilon = V + Ir$ **OR** calculates $R = 0.39 \text{ } (\Omega)$ ✓
Allow ruled line drawn through $(0.94, 0.37)$ and $(0.70, 0.65)$ ✓

Use of $\varepsilon = V + Ir$ **OR** $\varepsilon = I(R + r)$ ✓

Adds their gradient to read off at $I = 1.0 \text{ A}$ ✓ ✓

OR

Use of $y=mx+c$ with their gradient ✓

Intercept (c) determined ✓

1.4 (V) ✓

Ecf from (**c**). 3 sf max

3

[10]