

Name of the Student: _____

Max. Marks : 23 Marks

Time : 23 Minutes

Mark Schemes

Q1.

- (a) Idea that atoms gains energy (from beta particle) eg atoms excited or atoms/electrons moved to higher energy levels ✓

Idea that atom loses energy by emission of light/photons eg atoms de-excite or electrons move to lower energy levels ✓

Allow ionisation as named process

2

- (b) Use of $E = \frac{hc}{\lambda}$ OR use of $c = f\lambda$ and $E = hf$ ✓

Condone POT error for λ

$$3.2 \times 10^{-19} \text{ (J)} \quad \checkmark$$

Allow $3.1 \times 10^{-19} \text{ (J)}$ if 6.6×10^{-34} used

2

- (c) Use of $W = QV$ OR determines pd = 750 V ✓

$$1.2 \times 10^{-16} \text{ (J)} \quad \checkmark$$

2

- (d) Max 3 from: ✓ ✓ ✓

Attempt to count squares OR calculate unit area OR Statement that area under curve = charge flow

$$1 \text{ small square} = 2 \times 10^{-12} \text{ (C)} ; 1 \text{ large square} = 5 \times 10^{-11} \text{ (C)}$$

Counts number of squares/Determines area

Converts number of squares to charge

Accept 140 to 180 small or 5.5–7 large squares

Accept $\frac{1}{2}$ base \times height for triangle of base 12–16 ns and height 50 mA

Divides their total charge by 1.60×10^{-19}

$$2 \times 10^9 \quad \checkmark$$

Allow 1 sf answer

4

[10]

Q2.

- (a) Use of power equation

Or combination of power equation and $V = IR$

To get $R = 96 \, (\Omega)$. ✓

Must see some working

Do not allow reverse arguments

1

- (b) Either calculation of current through one lamp

Condone use of any other method eg use of power = 4.5 W and power equation.

And multiply by 3

OR

calculate total resistance ✓ (and use $V = IR$)

To give 0.38 A. ✓ (at least 2sf)

Allow ecf for their R from (a) used or their I

Use of 100 Ω gives 0.36 A (0.4A)

2

- (c) Evidence of equation to calculate area . ✓

$2.8 \times 10^{-8} \text{ m}^2$ ✓

Use of resistivity equation to get 49 Ω . ✓

Allow POT error in MP1

Evidence for MP2 may be in final answer

Accept 48 Ω

3

- (d) Total resistance = $46 + 46 + 100/3 = 125 \, \Omega$. ✓

Allow ecf for incorrect resistance

Calculation of circuit current = $12/125 = 0.096 \text{ A}$. ✓

operating current of lamp ($= 1.5/12 = 0.13$)/current for all 3 lamps to be fully on = 0.38 A. ✓

Yes demo works as lamps will be dimmer/ off (with constantan). ✓

If no other marks awarded, one mark each can be given for (max 2)

- *for resistance increases with length.*
- *Too much p.d. dropped across constantan*
- *Resistivity of constantan is greater than resistivity of copper*

For MP3 allow quoted comparison to previously calculated current in (b)

For MP4 allow ecf if answer is yes and is consistent with their calculation

4

- (e) **Advantage**

Zero resistance/resistivity. ✓

Reduce heat/energy transfer / power loss in cables ✓

Difficulty

Difficult to maintain low temperature (over long distances) ✓

Must be kept at/below the critical temperature. ✓

Ignore references to critical field.

Allow very low resistance

Max 3

[13]