

Name of the Student: _____

Max. Marks : 22 Marks

Time : 22 Minutes

Mark Schemes

Q1.

- (a) 0.5 mm [0.05 cm, 0.0005 m] ✓
only acceptable answers

1

- (b) 8.65 mm [0.865 cm, 0.00865 m] ₁ ✓

the micrometer reads zero when the jaws are closed ₂ ✓

only 3sf answers are acceptable for ₁ ✓

accept no zero error for ₂ ✓

2

- (c) $L = (403 - 289 =) 114 \text{ mm}$ ✓

1

- (d) absolute uncertainty = 1 mm ₁ ✓

$$\text{percentage uncertainty} = \frac{1}{114} \times 100 = 0.88\% \substack{2} \checkmark$$

accept 2 mm for ab. uncertainty ₁ ✓

allow ecf for wrong L and / or wrong ΔL

accept 1.75%

2

- (e) should move wire directly over / closer to scale on the ruler to avoid parallax error ✓
both statement and explanation required for this mark

1

- (f) five values of R/L correct, recorded to 3 sf [last row to 3sf or 4sf]; accept values in $\Omega \text{ cm}^{-1}$ ✓

mean based on first four rows only; result $9.94 \Omega \text{ m}^{-1}$ [$9.94 \times 10^{-2} \Omega \text{ cm}^{-1}$] ✓

L/cm	R/Ω	$(R/L)\Omega\text{m}^{-1}$
81.6	8.10	9.93
72.2	7.19	9.96
63.7	6.31	9.91
58.7	5.85	9.97

44.1	4.70	10.66 (10.7)
------	------	--------------

2

(g) cross-sectional area = $\frac{\pi d^2}{4}$ ₁✓

resistivity from $\frac{R}{L} \times A$, correct substitution of result from 01.6 ₂✓

1.10×10^{-6} ₃✓

$\Omega \text{ m}$ ₄✓

resistivity from $\frac{R}{L} \times \frac{\pi d^2}{4}$ earns ₁₂✓✓

allow ₂✓ if $\frac{R}{L}$ value is not based on mean or on a mean from all five rows of table in 01.6

condone 1.12×10^{-6} for ₃✓ if fifth row in 01.6 was not rejected

withhold ₃✓ for POT error

4

[13]

Q2.

- (a) A combination of resistors in series connected across a voltage source (to produce a required pd) ✓

Reference to splitting (not dividing) pd

1

- (b) When R increases, pd across R increases ✓

Pd across R + pd across T = supply pd ✓

So pd across T / voltmeter reading decreases ✓

Alternative:

$$\frac{R_1 \times V_{\text{tot}}}{R_1 + R_2}$$

Use of $V = \frac{R_1 \times V_{\text{tot}}}{R_1 + R_2}$ ✓

V_{tot} and R_2 remain constant ✓

So V increases when R_1 increases ✓

3

- (c) At higher temp, resistance of T is lower ✓

1

So circuit resistance is lower, so current / ammeter reading increases ✓

1

- (d) Resistance of T = 2500 Ω

Current through T = $V / R = 3 / 2500 = 1.2 \times 10^{-3} \text{ A}$ ✓

(Allow alternative using $V_1/R_1 = V_2/R_2$)

pd across R = $12 - 3 = 9 \text{ V}$

The first mark is working out the current

1

Resistance of R = $V / I = 9 / 1.2 \times 10^{-3} = 7500 \Omega$ ✓

The second mark is for the final answer

1

(e) Connect the alarm across R instead of across T ✓

allow: use a thermistor with a ptc instead of ntc.

1

[9]