

Name of the Student: \_\_\_\_\_

Max. Marks : 17 Marks

Time : 17 Minutes

Mark Schemes

**Q1.**

- (a) (i) pd across resistor =
- $12 - 4.5 = 7.5 \text{ V}$

C1

1

- (ii)
- $I = (\text{answer to (a) (i)})/67$
- (allow
- $12/7.5/4.5$
- for this mark)

C1

0.110/0.112 (A)

A1

2

- (b) (i)
- $360 + 67 (= 427)$
- seen

C1

 $V = 12 \times 360/(360 + 67)$ 

C1

10.1 V

A1

3

- (ii) substitution
- $P = V^2/R$
- allow
- $360 \Omega/67 \Omega$
- ;
- 
- 10 V, 10.1 V, 1.9 V, 2 V

C1

 $1.9^2/67$ 

C1

0.053

C1

W or  $\text{J s}^{-1}$ 

A1

4

- (c)
- $1/R = 1/570 + 1/360$

C1

220 [ $\Omega$ ]

C1

total  $R = 287 \Omega$

C1

42/41.7 mA  $4.2 \times 10^{-2}/4.17 \times 10^{-2}$

A1

4

(d) extra charge carriers released as temperature rises

B1

increased thermal agitation of atoms resists flow of charge carriers

B1

1<sup>st</sup> effect overwhelms 2<sup>nd</sup>

A1

3

[17]