

Name of the Student: _____

Max. Marks : 20 Marks

Time : 20 Minutes

Mark Schemes

Q1.

(a)

comparator



differential amplifier

inverting amplifier

non-inverting amplifier

1

(b) Photodiode current from graph = $80 \mu\text{A}$ ✓*Allow $\pm 5 \mu\text{A}$ in reading from the graph*Voltage across resistor V_R

$$V_R = I \times R = 80 \times 10^{-6} \times 39 \times 10^3$$

$$V_R = 3.12 \text{ V} \quad \checkmark$$

Allow a $V_R = 2.93 \text{ V}$ to 3.32 V

$$\text{Voltage at non-inverting pin } (V_+) = (5 - 3.12) = 1.88 \text{ V} \quad \checkmark$$

Allow a V_+ value of 2.07 V to 1.68 V


3

(c) Voltage at inverting pin (V_-) is 2.2 V ✓ $V_- > V_+$ so output is low / 0 V so LED will light / on ✓**First mark** is for correct value of (V_-)**Second mark** is for correct application / conclusion using $V_+ = 1.9 \text{ V}$ together with their value for (V_-)

2

[6]

Q2.

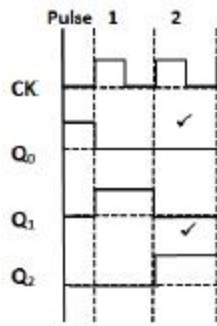


(a)

Flat line of Q_0 - 1 mark

Correct fall of Q_1 and rise of Q_2 - 1 mark

2

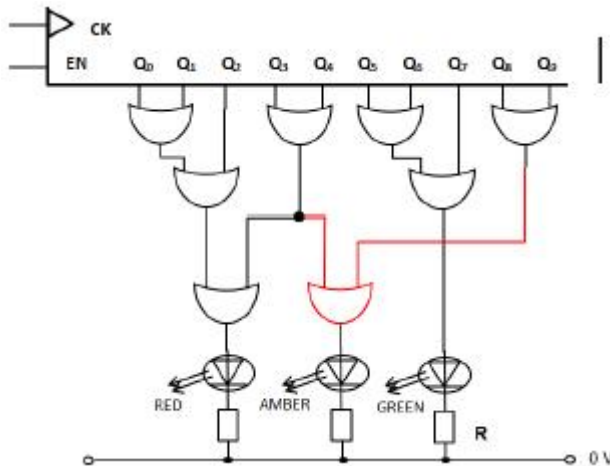

(b)

Logic OR gate correctly connected in position for 1 mark

1

(c) The ON time for the green LED is determined by:

the frequency of the clock ✓

the number of adjacent outputs that are OR'ed ✓

Accept reference to the period of the clock pulse.

2

(d) $R = V_R / I$; $R = (9 - 2.1) \text{ V}$ ✓ / 9 mA

$R = 6.9 \text{ V} / 9 \text{ mA}$; $R = 767 \Omega$ ✓

Minimum resistor value that can be used in order not to exceed 9 mA is 767 Ω .

The 720 Ω resistor range is (684 to 756) Ω and falls below this value so should not be used. ✓

OR

Calculation using 720 Ω $\pm 5\%$ Resistor range = (684 to 756) Ω ✓ leading to smallest current of 9.1 mA ✓

This current will exceed the permitted value of 9 mA. Don't use. ✓

1 One mark for voltage across the resistor

2 One mark for a suitable I-V-R calculation

³One mark for conclusion with reason.

Use of error range to give max resistance must be seen in either ₂ or ₃ for that mark to be awarded.

3

[8]

Q3.

(a) difference amplifier ✓

1

(b) $V_{\text{out}} = (V_+ - V_-) \times (R_f / R_{\text{in}})$

$V_{\text{out}} = (0 \text{ V} - 150 \text{ mV}) \times (1 \text{ M}\Omega / 100 \text{ k}\Omega)$ ✓

$V_{\text{out}} = -1.5 \text{ V}$ ✓

1 mark for the correct resistor substitution / resistor ratio (10)

1 mark for -1.5 V (must have correct sign)

2

(c) Signal 2 is subtracted from signal 1 by the difference amplifier ✓

Noise is common to both so will be reduced / eliminated when subtracted ✓

Signals will also be subtracted resulting in an addition (re-enforcement) of the signal. ✓

Accept arguments based on the 'phase' relationship

3

[6]