


Name of the Student: _____

Max. Marks : 20 Marks

Time : 20 Minutes

Q1.

- (a) Two logic inputs, **A** and **B**, feed into the logic circuit shown in **Figure 1**. The logic output from the circuit is **Q**.

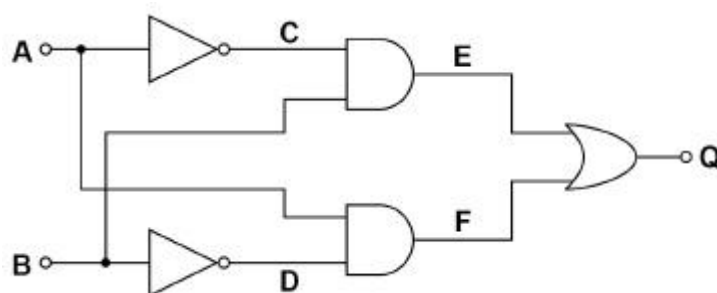Figure 1

Deduce the Boolean expression for the output of this logic circuit in terms of inputs **A** and **B**. Include all the logic operations that take place between the inputs and the output.

Q = _____**(2)**

- (b) The truth table shows some of the logic states for the logic gates in **Figure 1**.


Complete the truth table.

B	A	C	D	E	F	Q
0	0		1		0	0
0	1		1		1	1
1	0		0		0	1
1	1		0		0	0

(2)

- (c) **Figure 2** shows a different logic circuit that produces the same logic output as that of **Figure 1**.

Figure 2

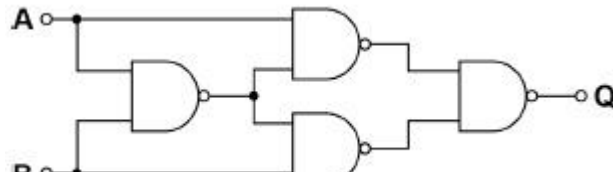

A manufacturer wants to produce a system that uses this logic function, but is undecided as to which circuit to use.

Suggest, giving reasons, **two** benefits of using the logic circuit in **Figure 2** compared to the logic circuit in **Figure 1**.

(2)

- (d) State the single logic gate that would perform the same logic function as the circuits shown in **Figure 1** and **Figure 2**.

(1)

(Total 7 marks)

Q2.


- (a) An ultrasound sensor produces an output that needs to be amplified to 3.0 V
The amplifier used has a voltage gain of 40

Calculate the input voltage V_{in} to the amplifier from the sensor.

$$V_{in} = \underline{\hspace{2cm}} \text{ V}$$

(1)

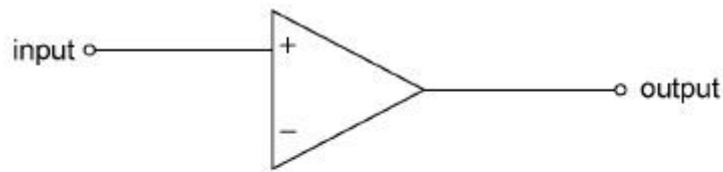- (b) An operational amplifier in non-inverting mode is used to amplify the output of the sensor. The partially completed circuit diagram is shown below.



Complete the circuit diagram above by adding and labelling two resistors, R_{in} and R_f , so that the operational amplifier is correctly configured in its non-inverting mode.

The power lines should not be shown in the completed diagram.

(2)

- (c) Determine, using resistors selected from the list below, how the voltage gain of 40 can be achieved by the non-inverting amplifier of the diagram.

1 k Ω 3.6 k Ω 10 k Ω 39 k Ω 150 k Ω

$R_{in} =$ _____ k Ω

$R_f =$ _____ k Ω

(2)

- (d) The ultrasound frequency detected by the sensor is 50 kHz
For this operational amplifier

$$\text{gain} \times \text{bandwidth} = 1.0 \text{ MHz}$$

Discuss whether this operational amplifier is suitable for amplifying the sensor's output voltage.
