Practice Question Set For A-Level

Subject: Physics

Paper-3 Topic: Section B (Section 13_ Electronics)



Name of the Student:_____

Max. Marks: 21 Marks Time: 21 Minutes

Mark Schemes

Q1.

(a)

(c)


Number shown on die	Logic inputs			Logic outputs						
	С	В	Α	L1	L2	L3	L4	L5	L6	L7
1	0	0	0	0	0	0	0	0	0	1
2	0	0	1	1	0	0	0	0	1	0
3	0	1	0	1	0	0	0	0	1	1
4	0	1	1	1	0	1	1	0	1	0
5	1	0	0	1	0	1	1	0	1	1
6	1	0	1	1	1	1	1	1	1	0
Reset 6 → 1										

One mark for each full pattern of **L1** and **L6**:

(b) L7 = NOT A; Accept: L7 = \overline{A}

1


2

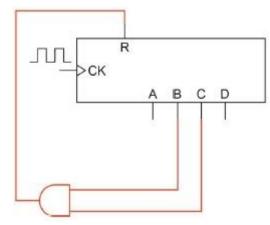

1 mark for reset condition from B and C 1 mark for use of a single 2-input AND gate

(accept correct implementation of the full reset code \overline{A} .B.C for 1 mark)

2

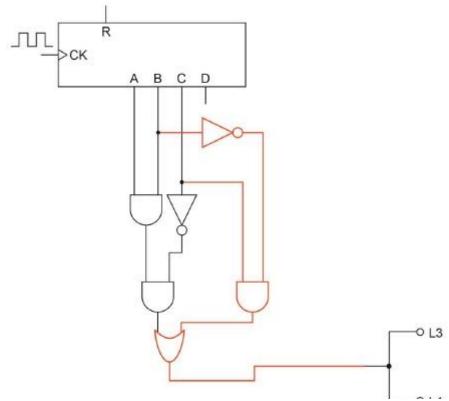

(d)

1 mark - NOT gate from B:

1 mark - OR gate connecting the two conditions:

[8]

3

Q2.

(a)
$$f = 1 / (2\pi \sqrt{LC})$$

$$C = 1/f^2 4\pi^2 L$$


$$C = 1/(910 \times 10^3)^2 \times 4 \times \pi^2 \times 1.1 \times 10^{-3}$$

C = 27.8 pF (accept 28pF)

Formula with correct substitution / evidence of correct working

Answer



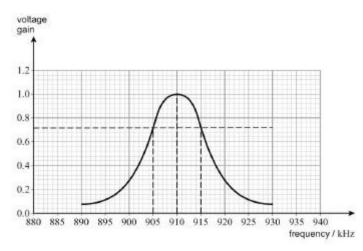

(b)

General shape around f_0 and to max of 1.0 on relative voltage gain axis

10 kHz bandwidth

1

Frequencies (905 – 910 – 915) kHz (identified / used)

1

(c) Smaller Q factor leads to:

(Any **two** from)

- (i) Broader bandwidth
- (ii) More noise / (hiss) detected
- (iii) Less selectivity
- (iv) More susceptible to crosstalk from neighbouring stations on the frequency spectrum.
- (v) Less gain due to energy loss / loss of signal detail

[7]

2

Q3.

(a) Period $T (= 11.3 - 3.2) = 8.1 \pm 0.2 \text{ ms.} \checkmark$

Number of revolutions per second $\left(=\frac{1}{T}=\frac{1}{8.1\times10^{-3}}\right)=120~(\pm~10)~({\rm rev~s^{-1}}).\checkmark$

(b) Signal is noisy **OR** output is not at appropriate levels for logic circuit. ✓

1

2

(c)
$$V_{\rm A} \left(= \frac{12}{12 + 8.2} \times 5 \right) = (+)2.97 \,\rm V$$

1

(d) Output pd switches between 0 and +5V. ✓
Output pd is inverted compared to input pd. ✓
Waveform has vertical sides cutting curve at about 3V. ✓

MAX 2

[6]