

Practice Question Set For A-Level
Subject : Physics
Paper-1 Topic : 3_ElectricCircuits

Name of the Student: _____

Max. Marks : 20 Marks

Time : 20 Minutes

Mark Schemes

Q1.

| Question Number | Answer | Mark |
|-----------------|--------|------|
| | C | 1 |

Q2.

| Question Number | Acceptable answers | Additional guidance | Mark | | |
|-----------------|--|---------------------|-----------|--|---|
| | <p>The only correct answer is B</p> <table><tr><td>decreases</td><td>increases</td></tr></table> | decreases | increases | <p>C and D are incorrect as the resistance decreases</p> <p>A is incorrect as n increases</p> | 1 |
| decreases | increases | | | | |

Q3.

| Question Number | Answer | Mark |
|-----------------|--------|------|
| | D | 1 |

Q4.

| Question Number | Acceptable answers | Additional guidance | Mark |
|-----------------|--|---------------------|------|
| | <p>The only correct answer is C</p> <p>A is not the correct answer, as I, n and e all constant.</p> <p>B is not the correct answer, as I, n and e all constant.</p> <p>D is not the correct answer, as I, n and e all constant.</p> | | 1 |

Q5.

| Question Number | Acceptable Answer | Additional Guidance | Mark |
|-----------------|---|---------------------|----------|
| | D Work done per unit charge to move a charge around a circuit. | | 1 |

Q6.

| Question Number | Acceptable answers | Additional guidance | Mark |
|-----------------|--------------------|---------------------|----------|
| | C | | 1 |

Q7.

| Question Number | Acceptable answers | Additional guidance | Mark |
|-----------------|---|---------------------|----------|
| | A uses the parallel resistors equation $\frac{1}{R_T} = \frac{1}{R} + \frac{1}{R} = \frac{2}{R}$ | $\frac{R}{2}$ | 1 |
| | B assumes resistors in parallel have the same total R as each individual R C is the addition of both resistances as if they were in series D is the product of both resistances | | |

Q8.

| Question number | Acceptable answers | Additional guidance | Mark |
|-----------------|--------------------|---------------------|----------|
| | D | | 1 |

Q9.

| Question Number | Answer | Mark |
|-----------------|----------|----------|
| | D | 1 |

Q10.

| Question Number | Answer | Mark |
|-----------------|----------|----------|
| | B | 1 |

Q11.

| Question Number | Answer | Mark |
|-----------------|--------|------|
| | C | 1 |

Q12.

| Question Number | Answer | Mark |
|-----------------|--------|------|
| | B | 1 |

Q13.

| Question Number | Answer | Additional Guidance | Mark |
|-----------------|-------------------------------------|--|----------|
| | B is the only correct answer | A is incorrect because amplitude does increase C is incorrect because rate of collision does increase D is incorrect because rate of energy transfer does increase | 1 |

Q14.

| Question Number | Answer | Mark |
|-----------------|--------|------|
| | A | 1 |

Q15.

| Question Number | Acceptable answers | Additional guidance | Mark |
|-----------------|--|--|----------|
| | <p>The only correct answer is B</p> <p><i>A is not correct because R decreases as more conduction electrons</i></p> <p><i>C is not correct because lattice vibrations not affected</i></p> <p><i>D is not correct because lattice vibrations not affected</i></p> | It increases because there is an increase in the number of conduction electrons. | 1 |

Q16.

| Question Number | Acceptable answers | Additional guidance | Mark |
|-----------------|--|---------------------|----------|
| | <p>The only correct answer is B</p> <p>A is not correct as the p.d. across the resistor will increase</p> <p>C is not correct as the resistance of the LDR will decrease</p> <p>D is not correct as the resistance of the LDR will decrease</p> | | 1 |

Q17.

| Question Number | Acceptable answers | Additional guidance | Mark |
|-----------------|--------------------|---------------------|----------|
| | B | | 1 |

Q18.

| Question Number | Answers | Additional Guidance | Mark |
|-----------------|---------|-----------------------------|------------|
| | B | the rate of flow of charge. | (1) |

Q19.

| Question Number | Answers | Additional Guidance | | Mark | | | | |
|-----------------|---------------------|--|----------|---------------------|----------|---------------|--|-----|
| | D | <table><tr><td>Gradient</td><td>Intercept on y-axis</td></tr><tr><td>negative</td><td>ε</td></tr></table> | Gradient | Intercept on y-axis | negative | ε | | (1) |
| Gradient | Intercept on y-axis | | | | | | | |
| negative | ε | | | | | | | |

Q20.

| Question Number | Answers | Additional Guidance | Mark |
|-----------------|---------|---------------------|------------|
| | D | 3W | (1) |