

Practice Question Set For A-Level
Subject : Physics
Paper-1 Topic : 3_ElectricCircuits

Name of the Student: _____

Max. Marks : 15 Marks

Time : 15 Minutes

Mark Schemes

Q1.

Question Number	Answer	Mark
	C	1

Q2.

Question Number	Acceptable answers	Additional guidance	Mark
	D		1

Q3.

Question Number	Acceptable answers	Additional guidance	Mark
	D In the dark the resistance of the LDR will be very large so practically all the potential difference of 6V will be across it.	a little below 6 V	1
	A assumes the resistance of the LDR decreases to almost zero B assumes the resistance of the LDR decreases a little C assumes the resistance of the LDR increases a little		

Q4.

Question Number	Answer	Mark
	C $\text{kg m}^2 \text{s}^{-3} \text{A}^{-2}$	1
	Incorrect Answers: A – Ω is not a base unit B – V is not a base unit D – C is not a base unit	

Q5.

Question Number	Answer	Mark
	D $\text{kgm}^2\text{s}^{-3}\text{A}^{-1}$	1
	Incorrect Answers: A – correct units but J and C are not base units B – correct units but J is not a base unit C – correct units but C is not a base unit	

Q6.

Question Number	Answer	Mark
	<p>The only correct answer is C $\frac{V}{RnAe}$ this comes from the rearrangement of $I = nqvA$, and substitution for I using $R = \frac{V}{I}$</p> <p>A is not correct because this answer is rearranged incorrectly B is not correct because this answer is rearranged incorrectly D is not correct because this answer is rearranged incorrectly</p>	1

Q7.

Question Number	Answer	Mark
	<p>D $\frac{mgh}{VIt}$</p> <p>Incorrect Answers: A – this answer is incorrect B – this answer is incorrect C – this answer is incorrect</p>	1

Q8.

Question Number	Answer	Mark
	<p>The correct answer is D</p> <p>Incorrect Answers:</p> <p>A – emf is a constant</p> <p>B – emf is a constant</p> <p>C – as resistance increases, the terminal p.d. increases</p>	1

Q9.

Question Number	Answer	Mark
	<p>C ammeter reading decreases, voltmeter reading increases</p> <p>A – the ammeter reading does not increase</p> <p>B – neither occurs</p> <p>D – the voltmeter reading does not decrease</p>	1

Q10.

Question Number	Acceptable answers	Additional guidance	Mark
	<p>The only correct answer is B</p> <p>A is not correct as $120\ \Omega / 3 = 40\ \Omega$</p> <p>C is not correct as $120\ \Omega / 3 = 40\ \Omega$</p> <p>D is not correct as $120\ \Omega / 3 = 40\ \Omega$</p>		1


Q11.

Question Number	Answer	Mark
	A	1


Q12.

Question Number	Answer	Mark
	C	1

Q13.

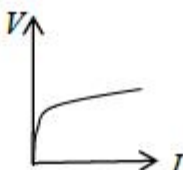Question Number	Acceptable Answer	Additional Guidance	Mark
	<p>C</p> 		1

Q14.

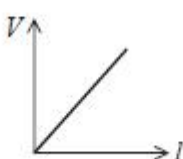Question Number	Acceptable Answer	Additional Guidance	Mark
	<p>A</p> 		1

Q15.

Question Number	Answer	Mark
	C The diode starts to conduct when the potential difference is about 0.7 V.	1
	<p>Incorrect Answers:</p> <p>A – The diode has zero resistance when connected in the forward direction</p> <p>B – The diode has zero resistance when connected in the reverse direction.</p> <p>D – The diode stops conducting when the potential difference is about –0.7 V.</p>	