Practice Question Set For A-Level

Subject: Physics

Paper-1 Topic : 3_ElectricCircuits



ame of the Student:

Max. Marks: 13 Marks

Time: 13 Minutes

Mark Schemes

Q1.

Question Number		Acceptable answers	Additional guidance				Mark
*	This question assesses a student's ability to show a coherent and logically structured answer with linkages and fully-sustained reasoning. Marks are awarded for indicative content and		IC points	IC mark	Max linkage mark available	Max final mark	
	for how the answer is structured and shows lines of reasoning.		6	4	2	6	ě.
			5	3	2	5	8
		llowing table shows how the marks be awarded for indicative content.	4	3	1	4	i:
	•	Use of $R = \rho l/A$	3	2	1	3	2
		the wider section will be half the	2	2	0	2	ý
	1	resistance of the narrow section	1	1	0	1	S). D:
	•	The p.d. will be divided into 0.5V across wide section and 1.0V across the narrow section	0	0	0	0	
	•	The potential will vary linearly along each resistance section (as <i>R</i> is proportional to <i>l</i>)					
	•	This is because current is constant throughout length					
	•	When the voltmeter is across the whole length it will read the p.d. across the cell/ 1.5V Or when the voltmeter terminals are together it will read 0 V					6

Question Number	Acceptable Answer	Additional Guidance	Mark	
(a)	 Use of R = V/I (1) Use of R = ρI/A (1) ρ = 1.34 × 10⁻⁶ Ωm (1) 	Example of calculation: $R = 1.50 \text{ V}/4.11 \text{ A} = 0.365 \Omega$ $\rho = RA/l = 0.365 \Omega \times \pi \times (1.82 \times 10^{-3}/2)^2$ $m^2/0.707 \text{ m}$ $\rho = 1.34 \times 10^{-6} \Omega \text{m}$		
(b)	 Calculates percentage uncertainty inlas 0.3% and in d as 1% (1) Calculates percentage uncertainty in resistivity by doubling that for d and adding that for l (1) Calculates range of values for ρ (1) Using these values the technician could not conclude whether the wire was Kanthal or Nichrome (1) 	$(0.2/70.7) \times 100 \% = 0.3 \%$ $(0.02/1.82) \times 100 \% = 1 \%$ %U in $\rho = 2 \times 1\% + 0.3 \% = 2.3 \%$ $1.34 \times 10^{-8} \times 0.0023 = 0.003$ $1.37 \times 10^{-8} > \rho > 1.31 \times 10^{-8}$ If answer to calculation is wrong, then credit can still be given for MP4 for		
		If no calculation is completed then MP4 cannot be awarded.	4	