

Name of the Student: _____

Max. Marks : 26 Marks

Time : 26 Minutes

Mark Schemes

Q1.

Question number	Acceptable answers	Additional guidance	Mark
	<p>Either</p> <ul style="list-style-type: none"> • Use $Q = 2.6$ to read time constant from graph (1) OR draw tangent to curve at $t = 0$ and obtain time constant from intercept on x axis (1) • $t = 17 - 18$ (ms) (1) • Use of $T = RC$ with their T (1) • $C = 0.019 - 0.021$ mF (1) <p>OR</p> <ul style="list-style-type: none"> • $Q_0 = 7$ (mC) read from graph (1) • Any corresponding values of Q and t read from graph (1) • Use of $Q = Q_0 e^{-t/RC}$ with their values for Q_0, Q and t (1) • $C = 0.0195 - 0.0196$ mF (1) <p>OR</p> <ul style="list-style-type: none"> • $Q_0 = 7$ (mC) read from graph (1) • $Q = 3.5$ (mC) when $T_{1/2} = 12.3$ (ms) (1) • Use of $T_{1/2} = RC \ln 2$ (1) • $C = 0.0195 - 0.0196$ mF (1) 	<p>Example of calculation:</p> <p>$T = 19$ (ms)</p> <p>$C = 19 \times 10^{-3} / 900 = 0.021$ mF</p>	4

Q2.

Question Number	Acceptable answers	Additional guidance	Mark
	<ul style="list-style-type: none"> • Use of $V = Q/4\pi\epsilon_0 r$ (1) • Conversion MeV to J (1) • Use of $V = W/Q$ (1) • $r = 3.0 \times 10^{-14} \text{ m}$ (1) 	<p>allow for $Q = 2$ or 79, accept $V = kQ/r$</p> <p>Must use $e = 1.6 \times 10^{-19} \text{ C}$ to convert atomic number to C</p> <p><u>Example of calculation:</u></p> $7.7 \times 10^6 \text{ eV} \times 1.6 \times 10^{-19} \text{ J eV}^{-1}$ $= 8.99 \times 10^9 \text{ N m}^2 \text{ C}^{-2} \times 2 \times 79 \times$ $(1.6 \times 10^{-19} \text{ C})^2 \div r$ $r = 2.27 \times 10^{-7} \div 7.7 \times 10^6$ $r = 2.95 \times 10^{-14} \text{ m}$	4

Q3.

Question Number	Acceptable Answer	Additional Guidance	Mark
	<ul style="list-style-type: none"> • Use of $Q = CV$ (1) • Use of $Q = Q_0 e^{-t/RC}$ (1) • $Q/Q_0 = 0.01$ (1) • $t = 11.6 \text{ ms}$ (1) • Use of $I = \frac{Q}{t}$ (1) • $I = 12 \text{ A}$ (1) 	<p><u>Example of calculation:</u></p> $Q = CV = 56 \times 10^{-6} \text{ F} \times 2500 \text{ V} = 0.14 \text{ C}$ $\ln\left(\frac{Q}{Q_0}\right) = e^{-t/RC}$ $\ln(0.01) = -\frac{t}{45 \Omega \times 56 \times 10^{-6} \text{ F}} \therefore t = 0.0116 \text{ s}$ $I = \frac{Q}{t} = \frac{0.14 \text{ s}}{0.0116 \text{ s}} = 12.1 \text{ A}$	(6)

Question Number	Answer	Mark
(a)(i)	Capacitor, resistor, supply and switch all in series (ignore voltmeter) Voltmeter directly across capacitor	(1) (1) 2
(a)(ii)	Datalogger allows large number of readings to be taken Or graph can be plotted directly/automatically Or simultaneous reading of t and V can be taken Or idea that people can't record quickly enough, (treat as neutral accuracy, precision misreading or human reaction time)	(1) 1
(b)	Use of $C = Q/V$ $Q = 5.0 \times 10^{-4} \text{ C}$ <u>Example of calculation</u> $Q = 100 \times 10^{-6} \text{ F} \times 5.0 \text{ V}$ $Q = 5.0 \times 10^{-4} \text{ C}$	(1) (1) 2
(c)(i)	Use of $I = \Delta Q / \Delta t$ e.c.f their value of C from (b) $I = 0.05 \text{ A}$ (accept recalculation of Q using $V = 4.90$ or 4.95 V) <u>Example of calculation</u> $I = 5.0 \times 10^{-4} \text{ C} / 10 \times 10^{-3} \text{ s}$ $I = 0.05 \text{ A}$	(1) (1) 2
(c)(ii)	tangent drawn at $t = 0$ $\Delta V / \Delta t = 2000 - 3300 \text{ V s}^{-1}$ Initial current = $0.22 - 0.28 \text{ A}$ (MP2 & 3 can be scored even if no tangent drawn) (No credit for exponential calculation) <u>Example of calculation</u> $\Delta V / \Delta t = 1.1 \text{ V} / 0.5 \text{ ms} = 2200 \text{ V s}^{-1}$ $I = (\Delta V / \Delta t) \times C$ $I = 2200 \text{ V s}^{-1} \times 100 \times 10^{-6} \text{ F}$ $I = 0.22 \text{ A}$	(1) (1) (1) 3
(c)(iii)	Use of $V = IR$ using answer from (ii) correct evaluation of R (5 V used with current range in (ii) gives $18 - 23 \Omega$) <u>Example of calculation</u> $5 \text{ V} = 0.22 \text{ A} \times R$ $R = 23 \Omega$	(1) (1) 2
Total for question		12