

Name of the Student: _____

Max. Marks : 16 Marks

Time : 16 Minutes

Mark Schemes

Q1.

- (a) a curve in the first and third quadrants only, passing through origin

1

decreasing gradient

1

- (b) any
- two**
- from:

- $I_1 = I_2 + I_3$
- $I_2 = I_3$
- $I_1 = 2I_2$
- $I_1 = 2I_3$

allow 1 mark for each correct description given in words

2

- (c)
- $3 = I^2 \times 12$

1

$$I = \sqrt{\left(\frac{3}{12}\right)}$$

1

$$I = 0.5 \text{ (A)}$$

1

$$Q = 0.5 \times 60 = 30$$

*allow Q =**their calculated I × 60*

1

$$Q_{\text{total}} = 60$$

allow an answer that is consistent with their calculated value of I

1

or

$$3 = I^2 \times 12 \text{ (1)}$$

$$I = \sqrt{\left(\frac{3}{12}\right)}$$

$$I = 0.5 \text{ (A) (1)}$$

$$I_{\text{total}} = 1.0 \text{ (A)} \text{ (1)}$$

allow $I_{\text{total}} = \text{their } I \times 2$

$$Q = 1.0 \times 60 = 60 \text{ (1)}$$

allow an answer that is consistent with their calculated value of I

coulombs **or** C

1

an answer of 60 scores 5 calculation marks

- (d) **Level 3:** Relevant points (reasons / causes) are identified, given in detail and logically linked to form a clear account.

5–6

Level 2: Relevant points (reasons / causes) are identified, and there are attempts at logically linking. The resulting account is not fully clear.

3–4

Level 1: Points are identified and stated simply, but their relevance is not clear and there is no attempt at logical linking.

1–2

No relevant content

0

Indicative content

- resistance of LDR changes when light intensity changes
- when light intensity increase resistance of LDR decreases
- overall resistance of circuit decreases
- potential difference across total resistance remains unchanged
- current in ammeter increases
- potential difference across fixed resistor increases
- potential difference across LDR decreases
- reading on the voltmeter decreases
- potential difference is shared between the components in series
- the lower the resistance of the LDR the smaller the share of the potential difference
- reading on the voltmeter decreases

[16]