

Name of the Student: _____

Max. Marks : 19 Marks

Time : 19 Minutes

Mark Schemes

Q1.

(a) 125

allow 1 mark for obtaining time period = 0.008 (s)

or

frequency = 1 / time period (or their calculated time period)

2

hertz

or

Hz

*do **not** accept hz*

1

(b) 50 (hertz)

1

[4]

Q2.

(a) alternates

accept switches

accept (constantly) changes

accept goes up and down

1

between positive and negative

1

(b) potential difference between the neutral and earth (terminal)

accept voltage for p.d

or potential of the neutral terminal with respect to earth

1

(c) (i) 0.025 (s)

1

(ii) 40 (Hz)


accept 1 ÷ their (a)(i)

1

[5]

Q3.

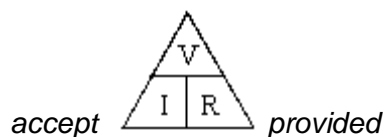- (a) (i) potential difference = current \times resistance
 accept voltage **or** pd for potential difference
 accept $V = I \times R$
 accept correct transformation
 do **not** accept $V = C \times R$
 do **not** accept $V = A \times R$



subsequent use of Δ correct
 do **not** accept an equation expressed in units

1

- (ii) 46

credit correct transformation for **1** mark
 allow 1 mark for use of 11.5 V or division of final resistance by 20
 a final answer of 920 gains **2** marks only

3

ohm(s)

accept symbol Ω
 do **not** accept Ω s
 unit / symbol mark can be awarded in (iii) provided unit / symbol is omitted in (ii)

1

- (iii) 920 (ohms) **or** their (a)(ii) \times 20

1


- (b) as temperature increases, resistance increases
 accept hotter for temperature increase
 do **not** accept a reference to resistance only i.e. it / resistance goes up

1

[7]

Q4.

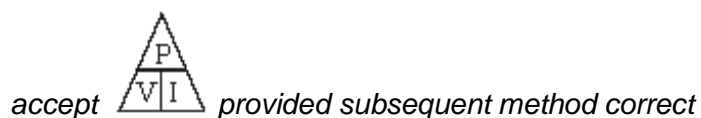- (i) power = potential difference \times current
 accept voltage for potential difference
 accept $P = V \times I$
or correct transposition



1

- (ii) 8

allow **1** mark for correct substitution or transformation **or** an answer
 2.67 / 2.7

2

[3]