

Name of the Student: \_\_\_\_\_

Max. Marks : 20 Marks

Time : 20 Minutes

Mark Schemes

**Q1.**

level drops as petrol used;  
 causes circuit resistance to increase;  
 causes current to decrease

*for 1 mark each*

**or** if change not specified;  
*(one correct and two vague statements gains 2 marks,  
 three vague statements gains 1 mark)*  
 e.g. level changes; )  
 so resistance changes; ) = 1 mark  
 so current changes )

**[3]****Q2.**

- (a) Current = 0.4A (1)  
 $R = V/I$  or  $240/0.4$  (1)  
 $R = 600 \text{ ohm}$  (1)

3

- (b) Doubles  
*gets 2 marks*

OR gets bigger  
*gets 1 mark*

2

- (c)  $P = V.I$  or  $240 \times 0.4$   
 $P = 96W$   
*for 1 mark each*

2

- (d)  $I = 0.2A$   
 $P = 48W$   
*for 1 mark each*  
*BUT may get equation mark here if not in (c)*

2

- (e)  $P = V.I.t$  (1)  
 $P = 240 \times 0.2 \times 6 \times 3600$   
**OR**  $P = 48 \times 6 \times 3600$   
*gets 1 mark*

$$P = 1036800 \text{ W}$$


*gets 1 mark*

3

[12]

**Q3.**

(a)

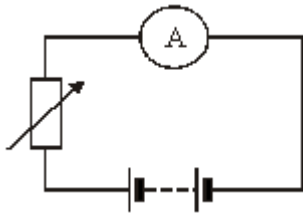

3

one mark for each symbol

allow more than 2 cells joined

*max. 2 marks if symbols incorrectly allow rheostat arrow in either direction*

(b) current will decrease

1

since resistance greater

1

[5]