

Name of the Student: _____

Max. Marks : 22 Marks

Time : 22 Minutes

Mark Schemes

Q1.

- (i) power = current \times voltage
 or any correctly transposed version
accept watts = amps \times volts
accept $P = IV$
do not credit $P = CV$
accept p.d. for voltage triangle acceptable only if used correctly in (ii)
- 1

- (ii) 2 000 000 (1)
 2000 kilowatts/kW (2)
 accept KW
- watts/W (1)
 2 megawatts/MW (2)
*do not credit mW (1) if correct method is clearly shown but answer is numerically incorrect **or** unit is absent **or** incorrect*
do not credit any working from an incorrect equation in (d)(i) but an appropriate unit should be credited
- 2

[3]**Q2.**

- (a) 0.9
- 1

1.1

accept the value of $A_4 + 0.2$

1

- (b) $V = I R$ **or** $12 = 0.6 R$ **or** $\frac{12}{0.6} = ?$
- accept $V = A R$*
 $V = I \times \text{ohm's sign}$
do not credit Ohm's law triangle
- 2

R = 20

correct numerical answer earns both marks

ohms

1

(c) $A_3 = 0.3$

$A_4 = 0.3$

accept the same numeric value as A_3

$A_5 = 0.5$

accept the value of $A_4 + 0.2$

3

[8]

Q3.

- (a) A = battery (of cells)/cells/cell
B = thermistor/temperature dependent resistor
C = transistor
D = LED/light emitting diode
E, F, G = resistors

each for 1 mark

5

- (b) *ideas that* (resistance) falls from 3000 to 200 units – ohms/ Ω – referred to at least once

each for 1 mark

(credit quickly at first then more slowly with 2 marks) (max 4 for part (b))

4

- (c) any figure in the range 22 – 26 (inclusive)

gains 1 mark

but 24

gains 2 marks

2

[11]