Practice Question Set For GCSE

Subject: Physics



Paper-1 Topic: GCSE Triple Science_Electricity (High Demand Questions)

Max. Ma	rks : 20 Marks Ti	me : 20 Minute
Q1.	diagram below shows part of a mains electricity lighting circuit in a house.	
	Neutral wire	
	Live wire —	
(a)	A fault in the switch caused a householder to receive a mild electric shock before device switched the circuit off.	a safety
	The mean power transfer to the person was 5.75 W.	
	The potential difference across the person was 230 V.	
	Calculate the resistance of the person.	
		<u> </u>
	Resistance =	Ω

(b) An electrician replaced the switch.

plain why.											
, ,											
current from go of the elec								les to	contra	act. T	he perso
e graph below						_		n a ne	rson o	an le	t ao den
frequency of	the el	ectricity	supp	oly.	ii oui	ioni a	Willo	ra po	10011	arr io	i go dop
	20 🖂										
	15										
Maximum										/	
current at which	10		\setminus								
a person can let go											
in mA											
	5										
	0	10	20	30	40	50	60	70	80	90	100
				F	requ	ency i	n hert	Z			
e UK mains fre	eauen	cv is 50	0 Hz.								
	-	-		1.112	- t (-				50 LL		
plain why it wo	oula be	e sater	ir tne	UK ma	ains ti	requei	ncy wa	as no t	50 H	Z.	
										-	

(c)

The electrician would have received an electric shock unless the circuit was disconnected from

(3)

(2)

Q2.

Figure 1 shows a person using an electric lawn mower.

Figure 1



(a) The lawn mower is connected to the mains electricity supply.


What is the frequency of the mains electricity supply in the UK?

(2)

The lawn mower has a switch on each side of the handle.

Figure 2 shows the circuit diagram for the lawn mower.

Figure 2

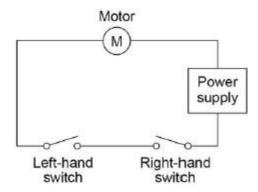

(b)	The motor in the lawn mower can only be turned on when the person using it holds the handle
	of the lawn mower with both hands.

Explain why.

;)	The power input to the motor is 1.8 kW	
	The resistance of the motor is 32 Ω	
	Calculate the current in the motor.	
	Current =	A
)	The useful power output from the motor is 1.5 kW	
	Calculate the time it takes for the motor to transfer 450 000 J of useful energy.	
		_
	Time =	seconds
		(Total 10 mar