

Name of the Student: _____

Max. Marks : 23 Marks

Time : 23 Minutes

Q1.


- (a) Complete the sentence. Choose answers from the box.

charge	potential difference	power	temperature	time
--------	-------------------------	-------	-------------	------

The current through an ohmic conductor is directly proportional to the _____ across the component, provided that the _____ remains constant.

(2)

- (b)
- Figure 1**
- shows a current – potential difference graph for a filament lamp.

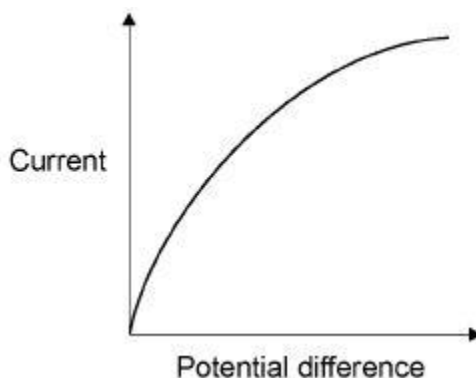Figure 1

Explain how the resistance of a filament lamp changes as the potential difference across it increases.

(3)

- (c) Many householders are replacing their filament lamps with LED lamps which are more energy

efficient.


What does more energy efficient mean?

(1)

A Light Dependent Resistor (LDR) is used to turn on an outside lamp when it gets dark.

Part of the circuit is shown in **Figure 2**.

Figure 2

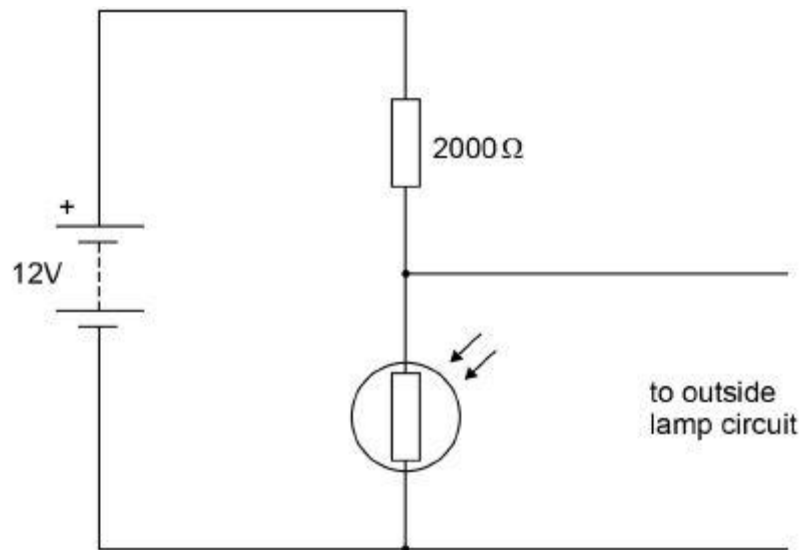

- (d) The light intensity decreases.

What happens to the potential difference across the LDR and the current in the LDR?

Potential difference _____

Current _____

(2)

- (e) What is the resistance of the LDR when the potential difference across it is 4 V?

Give a reason for your answer.

Explain your answer.

Resistance = _____ Ω

Reason _____

(2)

- (f) Calculate the current through the LDR when the resistance of the LDR is 5000 Ω .

Give your answer to 2 significant figures.

Current = _____ A

(4)

(Total 14 marks)

Q2.

The photograph below shows a coffee machine. The coffee machine uses an electric element to heat water.



- (a) The coffee machine has a metal case.

Why would it be dangerous for the live wire of the electric cable to touch the metal case?

(1)

- (b) The power output of the coffee machine is 2.53 kW.

The mains potential difference is 230 V.

Calculate the current in the coffee machine.

Current = _____ A

(3)

(c) The coffee machine heats water from 20 °C to 90 °C.

The power output of the coffee machine is 2.53 kW.

The specific heat capacity of water is 4200 J/kg °C.

Calculate the mass of water that the coffee machine can heat in 14 seconds.

Mass = _____ kg

(5)

(Total 9 marks)