

Name of the Student: _____


Max. Marks : 20 Marks

Time : 20 Minutes

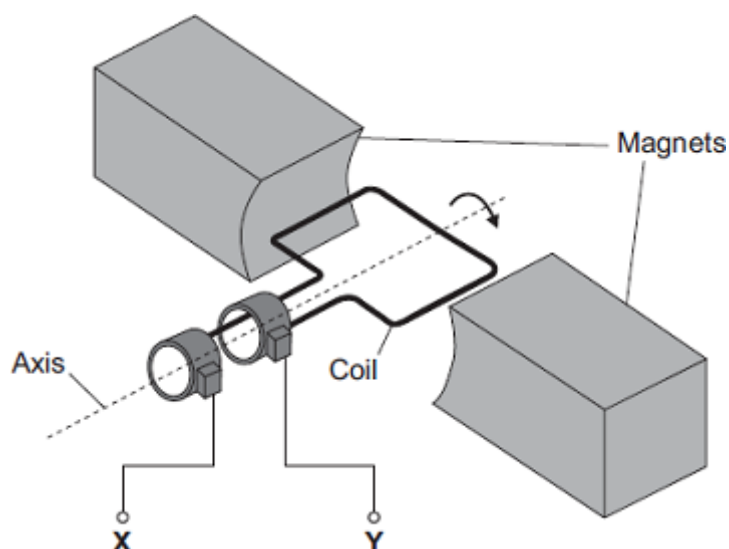Q1.

The diagram shows an a.c. generator.

The coil rotates about the axis shown and cuts through the magnetic field produced by the magnets.



- (a) (i) A potential difference is induced between **X** and **Y**.

Use the correct answer from the box to complete the sentence.

electric	generator	motor	transformer
-----------------	------------------	--------------	--------------------

This effect is called the _____ effect.

(1)

- (ii) What do the letters a.c. stand for?


(1)

- (iii) Name an instrument that could be used to measure the potential difference between **X** and **Y**.

(1)

- (b) **Graph 1** shows the output from the a.c. generator.

Graph 1

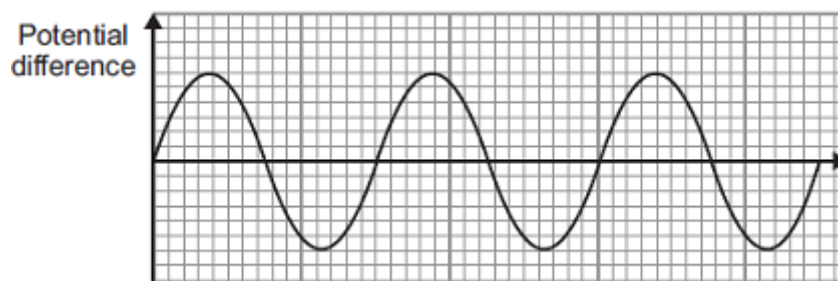

- (i) One of the axes on **Graph 1** has been labelled 'Potential difference'.

What should the other axis be labelled?

(1)

- (ii) The direction of the magnetic field is reversed.

On **Graph 1**, draw the output from the a.c. generator if everything else remains the same.

(2)

- (c) The number of turns of wire on the coil is increased. This increases the maximum induced potential difference.

State **two** other ways in which the maximum induced potential difference could be increased.

1. _____

2. _____

(2)

(Total 8 marks)

Q2.

The current in a circuit depends on the potential difference (p.d.) provided by the cells and the total resistance of the circuit.

- (a) Using the correct circuit symbols, draw a diagram to show how you would connect 1.5 V cells together to give a p.d. of 6 V.


(2)

- (b) **Figure 1** shows a circuit containing an 18 V battery.

Two resistors, **X** and **Y**, are connected in series.

- **X** has a resistance of $3\ \Omega$.
- There is a current of 2 A in **X**.

Figure 1

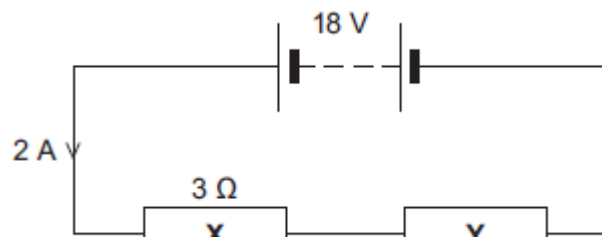

- (i) Calculate the p.d. across **X**.

P.d. across **X** = _____ V

(2)

- (ii) Calculate the p.d. across **Y**.

P.d. across **Y** = _____ V

(2)


- (iii) Calculate the total resistance of **X** and **Y**.

Total resistance of **X** and **Y** = _____ Ω

(2)

- (c) **Figure 2** shows a transformer.

Figure 2

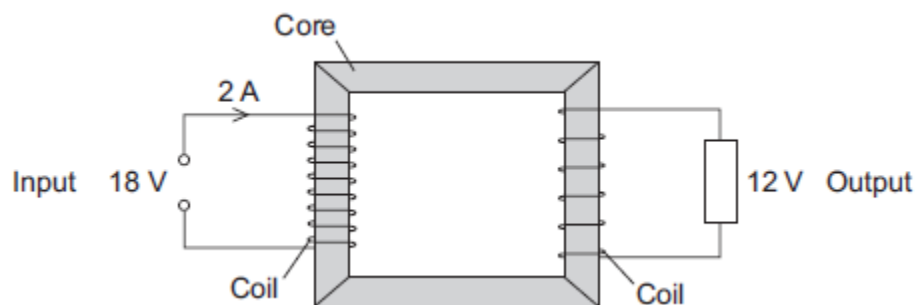

- (i) An 18 V battery could **not** be used as the input of a transformer.

Explain why.

(2)

- (ii) The transformer is 100% efficient.

Calculate the output current for the transformer shown in **Figure 2**.

Output current = _____ A

(2)

(Total 12 marks)