

Name of the Student: \_\_\_\_\_

Max. Marks : 20 Marks

Time : 20 Minutes

Mark Schemes

**Q1.**

(a) parallel 1

(b)  $S_1$  1(c)  $S_1, S_2$  and  $S_3$  1
 (d) energy transferred = power  $\times$  time  
 or  
 $E = P \times t$  1
(e)  $3600 = 1200 \times t$  1

$$t = \frac{3600}{1200}$$
 1

$$t = 3 \text{ (s)}$$
 1

 (f)  1
**[8]****Q2.**
 (a) A: transmission / power cables  
     *allow transmission / power lines*  
     *allow cables*  
     *ignore wires* 1

 B: step-down transformer 1

(b) less thermal energy is transferred to the surroundings. 1

- (c) charge flow = 500 000 000 1
- charge flow = 20 000 (C) 1
- (d) total current = 7.20 (A) 1
- $P = 230 \times 7.20$   
*allow a correct substitution of an incorrect total current* 1
- $P = 1656$  (W)  
*allow a correct calculation using an incorrect total current* 1
- (e) dishwasher 1
- has the largest current  
**or**  
 has the largest power (input) 1
- (f)  $E = 600 \times 32\,000\,000$  1
- $E = 19\,200\,000\,000$  (J)  
**or**  
 $E = 1.92 \times 10^{10}$  (J) 1

[12]