

Name of the Student: _____

Max. Marks : 26 Marks

Time : 26 Minutes

Mark Schemes


Q1.

- (a) correct circuit symbol

1

3 cells joined in series in correct orientation

e.g.

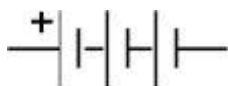

ignore absence of + symbol

1

- (b) $R = \frac{12}{1.6}$

1

$$R = 7.5 (\Omega)$$

1

an answer of 7.5 (Ω) scores 2 marks

- (c) 4.0 (Ω)

allow their answer to part (b) – 3.5 correctly calculated

1

- (d) it decreases

1

the current would be higher (for the same p.d.)

reason only scores if correct box is chosen

or

more than one path for charge to flow

allow current for charge

or

total resistance is always less than the smallest individual resistance

1

[7]

Q2.

- (a) 

1

(b) $E = 13 \times 230$

1

$E = 2990 \text{ (J)}$

1

an answer 2990 (J) scores 2 marks

(c) charge flow = current \times time

allow $Q = It$

1

(d) $1.52 = I \times 0.40$

1

$I = \frac{1.52}{0.40}$

1

$I = 3.8 \text{ (A)}$

1

an answer of 3.8 (A) scores 3 marks

(e) $E = 0.00175 \times 205\,000$

1

$E = 359 \text{ (J)}$

allow an answer that rounds to 360 (J) for 2 marks

1

an answer of 359 (J) scores 2 marks

[9]

Q3.

(a) $P = \frac{120\,000}{8.0}$

1

$P = 15\,000 \text{ (W)}$

1

an answer of 15 000 (W) scores 2 marks

(b) energy is transferred in heating the surroundings

1

friction causes energy to be transferred in non-useful ways

1

(c) the switches are in parallel

1

(so) closing either switch completes the circuit

1

(d) gravitational potential energy = mass \times gravitational field strength \times height

allow $E_p = m g h$

1

(e) $E_p = 280 \times 9.8 \times 14$

1

$$E_p = 38\,416 \text{ (J)}$$

1

$$E_p = 38\,000 \text{ (J)}$$

*an answer that rounds to 38 000 scores **2** marks*

1

*an answer of 38 000 scores **3** marks*

[10]