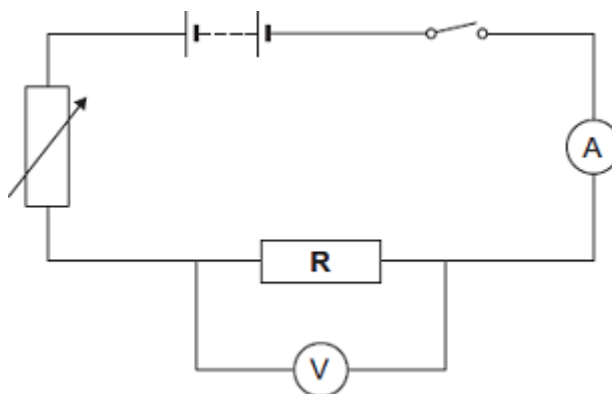


Max. Marks : 22 Marks

Time : 22 Minutes

Q1.

- (a) A resistor is a component that is used in an electric circuit.



- (i) Describe how a student would use the circuit to take the readings necessary to determine the resistance of resistor **R**.

This image shows a single sheet of white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page. There are no margins, text, or other markings on the paper.

- (ii) Explain why the student should open the switch after each reading.

(2)

- (iii) In an experiment using this circuit, an ammeter reading was 0.75 A.
The calculated value of the resistance of resistor **R** was 16 Ω .

What is the voltmeter reading?

Voltmeter reading = _____ V

(2)

- (iv) The student told his teacher that the resistance of resistor **R** was 16 Ω .

The teacher explained that the resistors used could only have one of the following values of resistance.

10 Ω 12 Ω 15 Ω 18 Ω 22 Ω

Suggest which of these resistors the student had used in his experiment.

Give a reason for your answer.

(2)

- (b) The diagram shows a fuse.




Describe the action of the fuse in a circuit.

(3)
(Total 15 marks)

Q2.

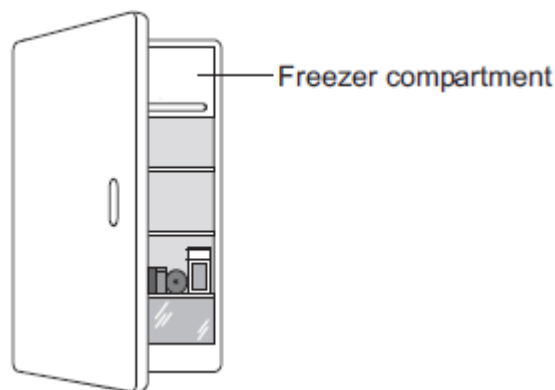- (a) The figure below shows a fridge with a freezer compartment.

The temperature of the air inside the freezer compartment is -5°C .



Use the correct answer from the box to complete each sentence.

Each answer may be used once, more than once or not at all.

decreased	unchanged	increased
-----------	-----------	-----------

When the air near the freezer compartment is cooled, the energy of the air particles is _____.

The spaces between the air particles are _____.

The density of the air is _____.

(3)

- (b) The table below shows some information about three fridges, **A**, **B** and **C**.

The efficiency of each fridge is the same.

Fridge	Volume in litres	Energy used in one year in kWh
A	232	292
B	382	409
C	622	524

- (i) Which fridge, **A**, **B** or **C**, would cost the least to use for 1 year?

Give **one** reason for your answer.

(2)

- (ii) A householder looks at the data in the table above.

What should she conclude about the pattern linking the volume of the fridge and the energy it uses in one year?

(1)

- (iii) The householder could not be certain that her conclusion is correct for all fridges.

Suggest **one** reason why not.

(1)

(Total 7 marks)