

Name of the Student: _____


Max. Marks : 17 Marks

Time : 17 Minutes

Mark Schemes

Q1.

(a)

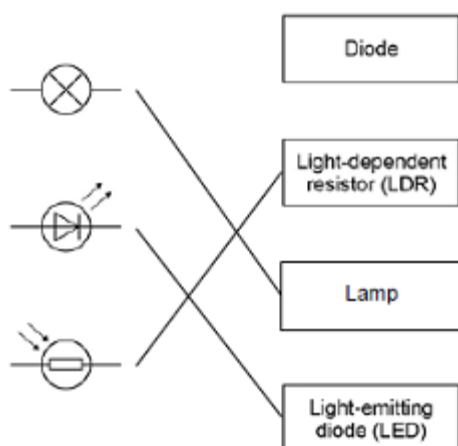

allow 1 mark for each correct line if more than one line is drawn from any symbol then all of those lines are wrong

3

(b) (i) half

1

(ii) 3(V)

1

(iii) V_1

1

(c) (i) potential difference / voltage of the power supply
 accept the power supply
 accept the voltage / volts
 accept number of cells / batteries
 accept (same) cells / batteries
 do not accept same ammeter / switch / wires

1

(ii) bar drawn – height 1.(00)A
 ignore width of bar
 allow 1 mark for bar shorter than 3^d bar

2

(iii) as the number of resistors increases the current decreases

1

[10]

Q2.

- (a) (i) temperature (increase) and time switched on are directly proportional
accept the idea of equal increases in time giving equal increases in temperature

answers such as:

- *as time increases, temperature increases*
- *positive correlation*
- *linear relationship*
- *temperature and time are proportional*

score 1 mark

2

- (ii) any **one** from:

"it" refers to the metal block

- *energy transfer (from the block) to the surroundings*
accept lost for transfer
accept air for surroundings
- *(some) energy used to warm the heater / thermometer (itself)*
accept takes time for heater to warm up
- *(metal) block is not insulated*

1

- (iii) 15 000

allow 1 mark for correct substitution, ie 50×300 provided no subsequent step shown

2

- (b) lead

reason only scores if lead is chosen

1

needs least energy to raise temperature by 1°C

accept needs less energy to heat it (by the same amount)
lowest specific heat capacity is insufficient

1

[7]