


Name of the Student: _____

Max. Marks : 19 Marks

Time : 19 Minutes

Q1.

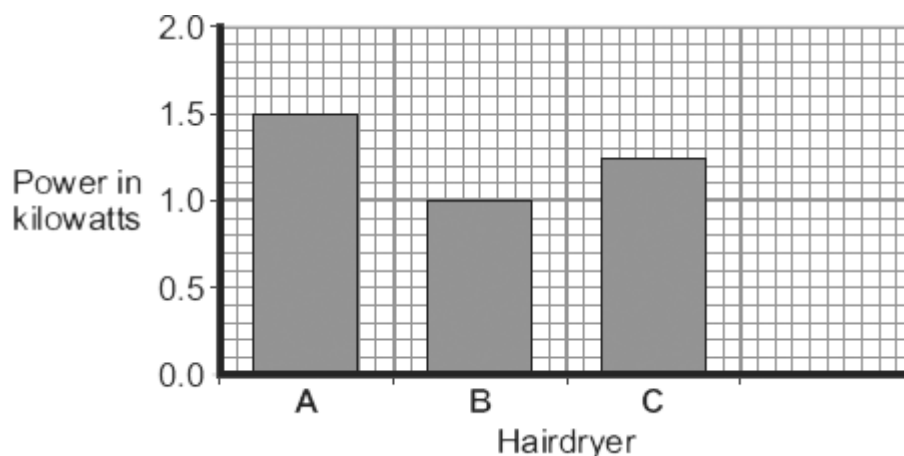- (a) The bar chart shows the power of three different electric hairdryers.



- (i) Which
- one**
- of the hairdryers,
- A**
- ,
- B**
- or
- C**
- , would transfer the most energy in 5 minutes?

Write the correct answer in the box.

(1)

- (ii) A small 'travel' hairdryer has a power of 500 watts.

Draw a fourth bar on the bar chart to show the power of the 'travel' hairdryer.

(1)

- (b) A family shares the same hairdryer.

The hairdryer has a power of 1.2 kW. The hairdryer is used for a total of 2 hours each week.

- (i) Calculate how many kilowatt-hours (kWh) of energy the hairdryer transfers in 2 hours.

Show clearly how you work out your answer.

Energy transferred = _____ kWh

(2)

- (ii) Electricity costs 15 pence per kWh.

Calculate the cost of using the hairdryer for 2 hours.

Show clearly how you work out your answer.


Cost = _____ pence

(2)

(Total 6 marks)

Q2.

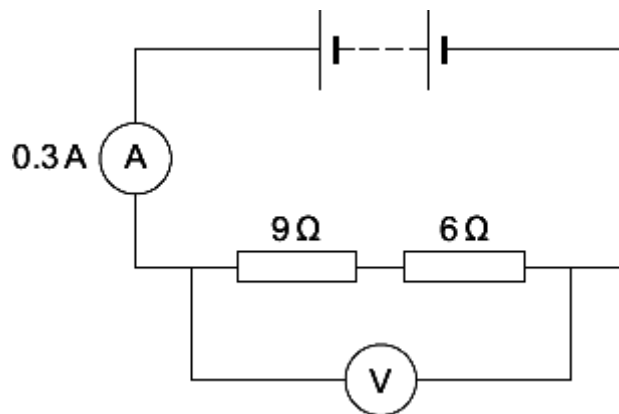- (a) The diagram shows a simple circuit.



- (i) Calculate the total resistance of the two resistors in the circuit.

Total resistance = _____ Ω

(1)

- (ii) Calculate the reading on the voltmeter.

Show clearly how you work out your answer.

Voltmeter reading = _____ V

(2)

- (iii) Draw a ring around the correct answer in the box to complete the sentence.

Replacing one of the resistors with a resistor of higher value will

decrease
not change
increase


the reading on the ammeter.

(1)

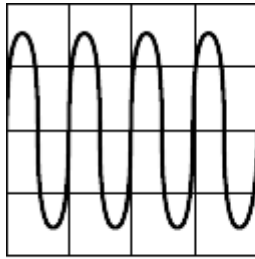
- (b) The voltmeter in the circuit is replaced with an oscilloscope.

Which one of the diagrams, **X**, **Y** or **Z**, shows the trace that would be seen on the oscilloscope?


Write your answer, **X**, **Y** or **Z**, in the box.



X

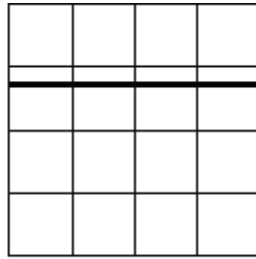

Y

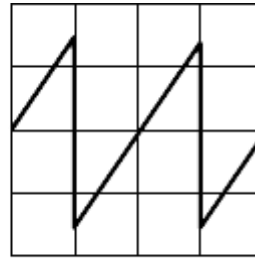

Z

Diagram




Give a reason for your answer.

(2)

(Total 6 marks)

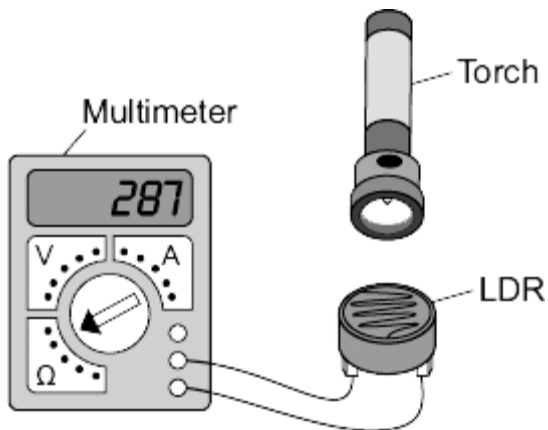Q3.


A student used the apparatus below to find out how the resistance of a light-dependent resistor (LDR) depends on light intensity.



The resistance of the LDR was measured directly using a multimeter.

- (a) (i) Which **one** of the following is the correct circuit symbol for a LDR?

Draw a ring around your answer.

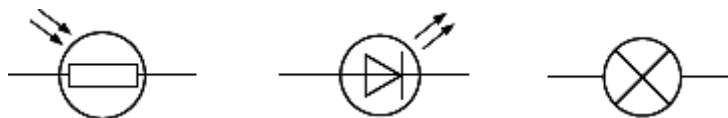


(1)

- (ii) Name **one** factor that will affect the intensity of the light hitting the LDR.

(1)

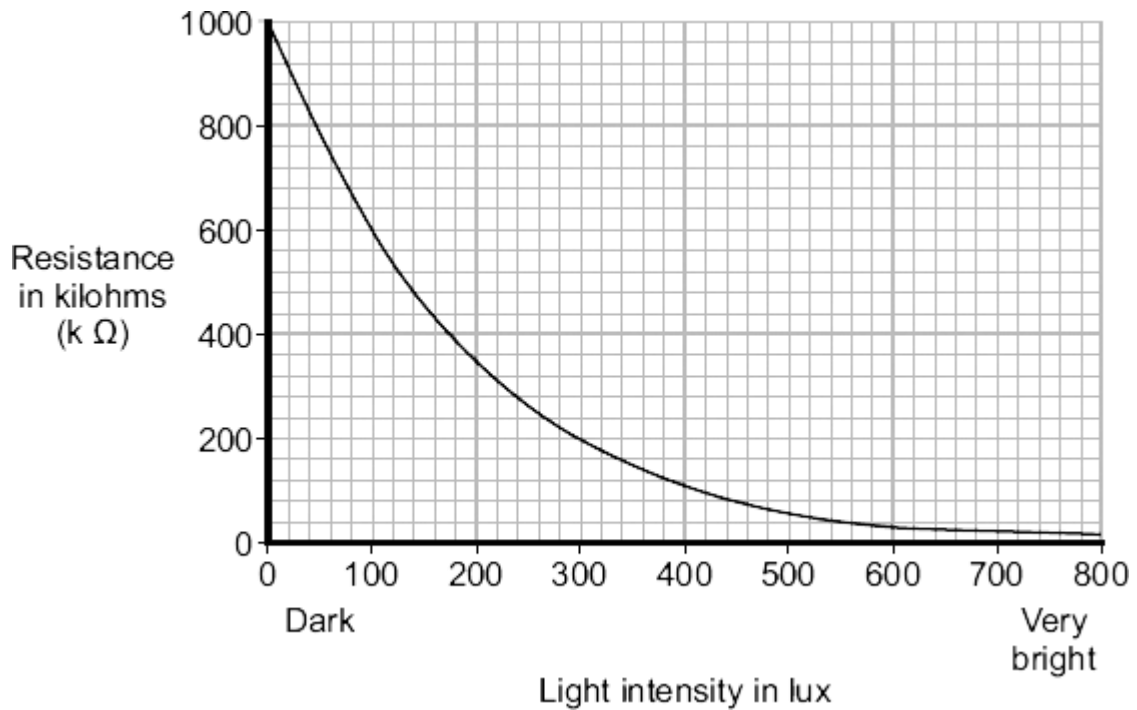- (b) The manufacturer of the LDR provides data for the LDR in the form of a graph.



Describe how the resistance of the LDR changes when the light intensity increases from 100 lux to 300 lux.

(2)

- (c) The student only obtained three results. These are given in the table.

Light intensity	Resistance in kilohms
Dark	750
Bright	100
Very bright	1

- (i) The student could **not** use the results to draw a line graph. Why not?

(1)

- (ii) Do the student's results agree with the data the manufacturer provided?

Draw a ring around your answer.

YES

NO

Give a reason for your answer.

(1)

(d) Which **one** of the following circuits probably includes a LDR?

Tick (✓) **one** box.

A circuit that automatically switches outside lights on when it gets dark.

☐

A circuit that automatically switches central heating on and off.

☐

A circuit that automatically turns lights off when no one is in the room.

☐

(1)

(Total 7 marks)