

Name of the Student: \_\_\_\_\_

Max. Marks : 18 Marks

Time : 18 Minutes

Mark Schemes

**Q1.**

(a)  $P = V \times I$

1

(b)  $4.4 = 40 \times I$

1

$$I = \frac{4.4}{40}$$

1

$$I = 0.11 \text{ (A)}$$

1

(c) 
$$\text{efficiency} = \frac{\text{useful power output}}{\text{total power input}}$$

1

(d) 
$$0.85 = \frac{P}{4.0}$$

1

$$P = 0.85 \times 4.0$$

1

$$P = 3.4 \text{ (W)}$$

1

**[8]****Q2.**

- (a)
- Level 3:**
- The method would lead to the production of a valid outcome. All key steps are identified and logically sequenced.

5-6

**Level 2:** The method would not necessarily lead to a valid outcome. Most steps are identified, but the plan is not fully logically sequenced.

3-4

**Level 1:** The method would not lead to a valid outcome. Some relevant steps are identified, but links are not made clear.

1-2

No relevant content

0

**Indicative content**

- measure the current in **R** using the ammeter
- measure the p.d. across **R** using the voltmeter
- vary the resistance of the variable resistor (or vary the number of cells or use a variable power supply)
- record a range of values of current and p.d.
  
- ensure current is low to avoid temperature increase
- switch circuit off between readings
- reverse connection of **R** to power supply
- repeat measurements of I and V in negative direction
- plot a graph of current against p.d.

(b) current and p.d. would not be directly proportional

**or**

I-V graph would not be straight

**or**

I-V graph would be curved

1

(because) resistance of **R** would increase

1

(c) 0.2 (A)

1

(d) any **one** from:

- less chance of misreading
- no parallax error

*allow position of eye(s) does not affect reading*

- it can give a reading closer to the true value

*allow 'it is more accurate'*

*ignore 'no human error' ignore 'easier to read'*

1

**[10]**