

Name of the Student: _____

Max. Marks : 21 Marks

Time : 21 Minutes

Q1.

The photograph below shows an electric car being recharged.



- (a) The charging station applies a direct potential difference across the battery of the car.

What does 'direct potential difference' mean?

(1)

- (b) Which equation links energy transferred (E), power (P) and time (t)?

Tick (✓) **one** box.

energy transferred = $\frac{\text{power}}{\text{time}}$

☐

energy transferred = $\frac{\text{time}}{\text{power}}$

☐

energy transferred = power \times time

☐

energy transferred = power² \times time

☐

(1)

- (c) The battery in the electric car can store 162 000 000 J of energy.

The charging station has a power output of 7200 W.

Calculate the time taken to fully recharge the battery from zero.

Time taken = _____ s

(3)

- (d) Which equation links current (I), potential difference (V) and resistance (R)?

Tick (✓) **one** box.

$I = V \times R$

☐

$I = V^2 \times R$

☐

$R = I \times V$

☐

$V = I \times R$

☐

(1)

- (e) The potential difference across the battery is 480 V.

There is a current of 15 A in the circuit connecting the battery to the motor of the electric car.

Calculate the resistance of the motor.

Resistance = _____ Ω (3)

(f) Different charging systems use different electrical currents.

- Charging system **A** has a current of 13 A.
- Charging system **B** has a current of 26 A.
- The potential difference of both charging systems is 230 V.

How does the time taken to recharge a battery using charging system **A** compare with the time taken using charging system **B**?

Tick (✓) **one** box.

Time taken using system **A** is half the time of system **B** ☐

Time taken using system **A** is the same as system **B** ☐


Time taken using system **A** is double the time of system **B** ☐

(1)
(Total 10 marks)

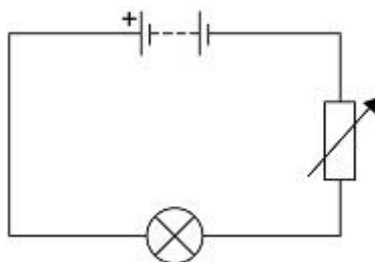Q2.

A student investigated how the current in a filament lamp varied with the potential difference across the filament lamp.

The diagram below shows part of the circuit used.




(a) Complete above diagram by adding an ammeter and a voltmeter.

Use the correct circuit symbols.

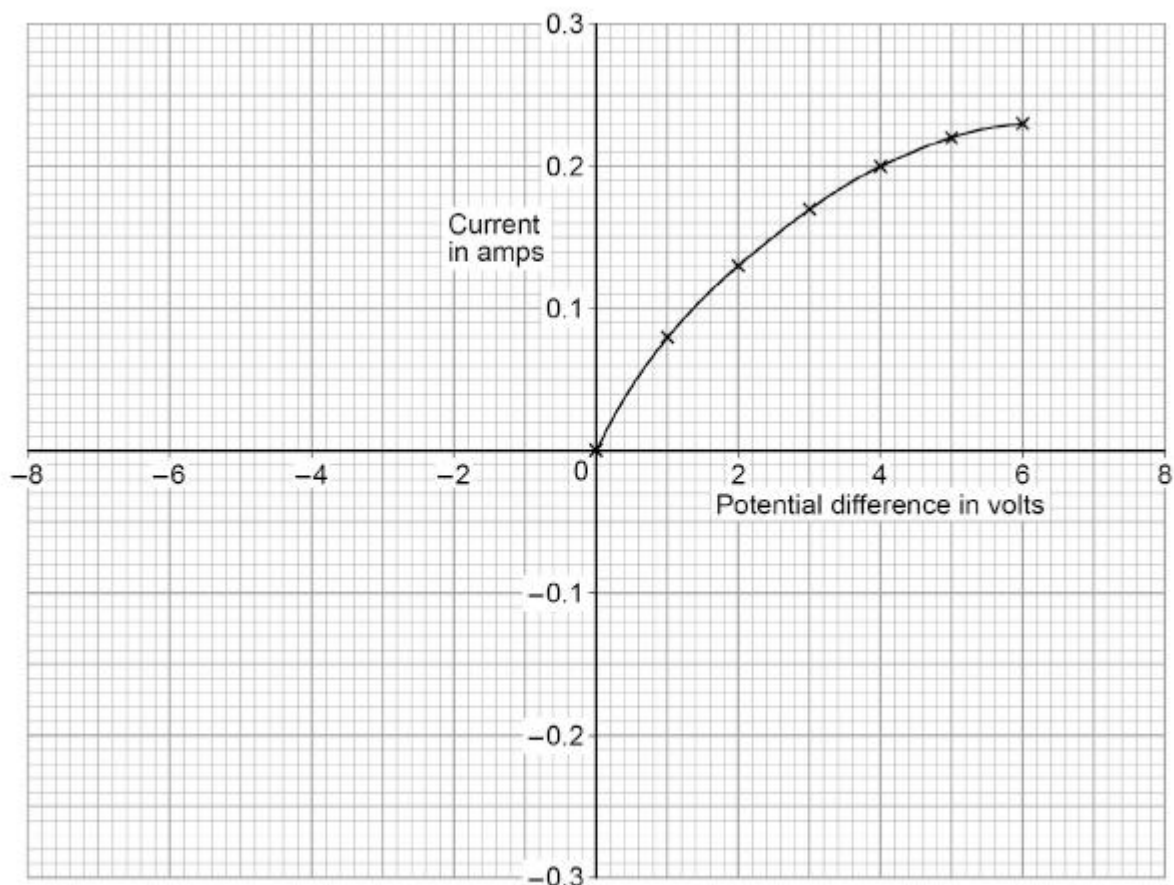(3)

The graph below shows some of the results.



- (b) The student reversed the connections to the power supply and obtained negative values for the current and potential difference.

Draw a line on the graph to show the relationship between the negative values of current and potential difference.

(2)

- (c) Write down the equation which links current (I), potential difference (V) and resistance (R).

(1)

- (d) Determine the resistance of the filament lamp when the potential difference across it is 1.0 V.

Use data from the graph above.

Resistance = _____ Ω

(4)

- (e) A second student did the same investigation. The ammeter used had a zero error.

What is meant by a zero error?

(1)
(Total 11 marks)