

Name of the Student: _____

Max. Marks : 25 Marks

Time : 25 Minutes

Q1.

Electrical circuits have resistance.

- (a) Draw a ring around the correct answer to complete the sentence.

When the resistance of a circuit increases, the current in the circuit

decreases. increases. stays the same.

(1)

- (b) Use the correct answer from the box to complete each sentence.

a filament bulb	an LED	an LDR
-----------------	--------	--------

An electrical component which has a resistance that increases as the temperature increases is _____ .

An electrical component which emits light only when a current flows through it in the forward direction is _____ .

(2)

- (c) When some metals are heated the resistance of the metal changes.

The equipment for investigating how the resistance of a metal changes when it is heated is shown in the diagram.


(6)

- (d) The table shows some data for samples of four metals **P**, **Q**, **R** and **S**.

The metal samples all had the same cross-sectional area and were the same length.

Metal sample	Resistance at 0°C in ohms	Resistance at 100°C in ohms
P	4.05	5.67
Q	2.65	3.48
R	6.0	9.17
S	1.70	2.23

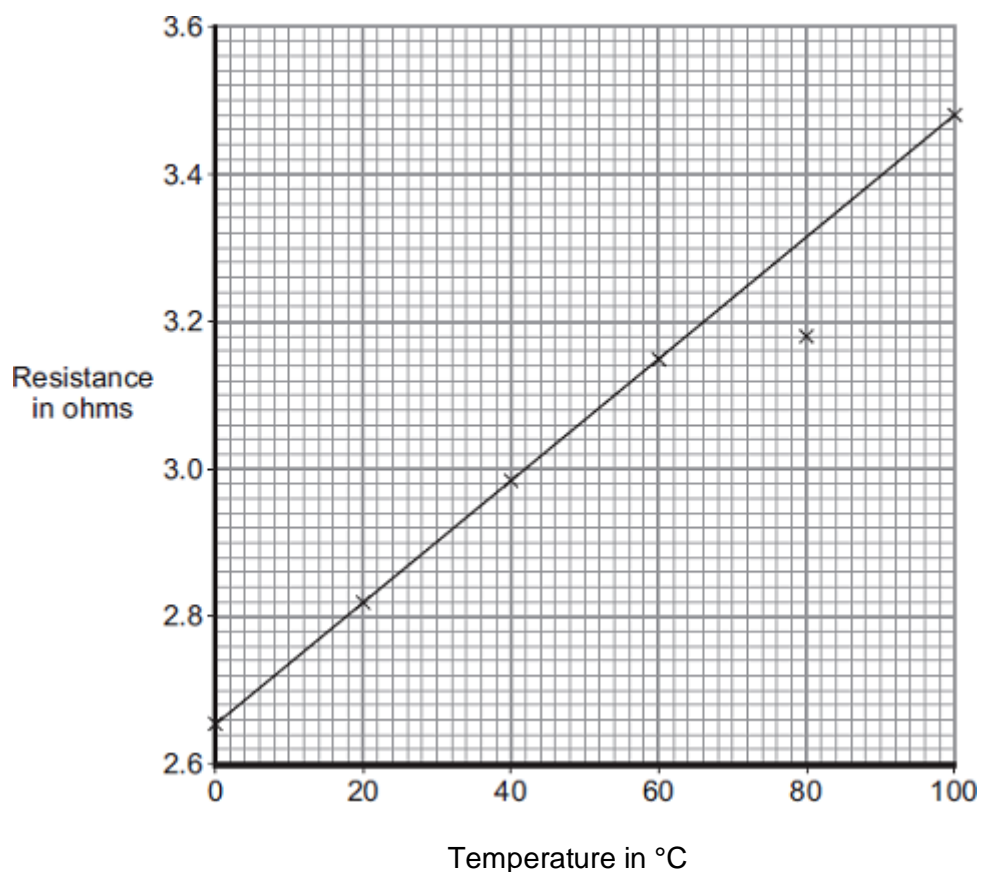A graph of the results for one of the metal samples is shown.



- (i) Which metal sample, **P**, **Q**, **R** or **S**, has the data shown in the graph?

(1)


(ii) One of the results is anomalous. Circle this result on the graph.

(1)

(iii) Suggest a reason for the anomalous result.

(1)

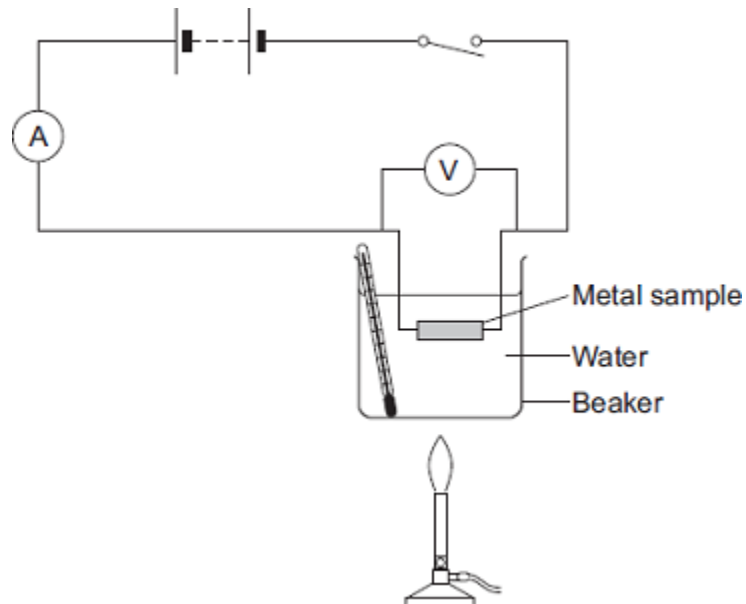(iv) The same equipment used in the investigation could be used as a thermometer known as a 'resistance thermometer.'



Suggest **two** disadvantages of using this equipment as a thermometer compared to a liquid-in-glass thermometer.

1. _____


2. _____

(2)

(Total 14 marks)

Q2.

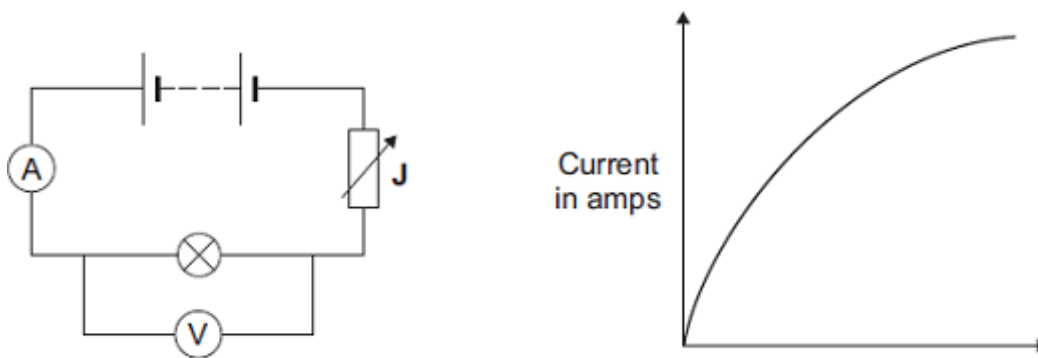- (a) The diagram shows the circuit used to obtain the data needed to plot the current–potential difference graph for a filament bulb.



- (i) Why is the component labelled 'J' included in the circuit?

(1)

- (ii) The resistance of the bulb increases as the potential difference across the bulb increases. Why?

(1)

- (iii) The bulb is at full brightness when the potential difference across the bulb is 12 V. The current through the bulb is then 3 A.

Calculate the power of the bulb when it is at full brightness and give the unit.

Power = _____

(3)

- (b) *In this question you will be assessed on using good English, organising information clearly and using specialist terms where appropriate.*

The table gives data about two types of light bulb people may use in their homes.

Type of light bulb	Energy efficiency	Cost of one light bulb	Average lifetime in hours
Halogen	10%	£1.95	2 000
Light Emitting Diode (LED)	32%	£11.70	36 000

Both types of light bulb produce the same amount of light.

Evaluate, in terms of cost and energy efficiency, the use of the two types of light bulb.

To gain full marks you must compare both types of light bulb and conclude which light bulb would be the best to use.

(6)
(Total 11 marks)