

Name of the Student: \_\_\_\_\_

Max. Marks : 18 Marks

Time : 18 Minutes

Mark Schemes

**Q1.**

- (a) attempt to draw four cells in series

1

*correct circuit symbols**circuit symbol should show a long line and a short line, correctly joined together**example of correct circuit symbol:*

1

- (b) (i) 6 (V)

*allow 1 mark for correct substitution, ie* *$V = 3 \times 2$  scores 1 mark**provided no subsequent step*

2

- (ii) 12 (V)

*ecf from part (b)(i)**18 – 6***or***18 – their part (b)(i) scores 1 mark*

2

- (iii) 9 (
- $\Omega$
- )

*ecf from part (b)(ii) correctly calculated**3 + their part (b)(ii) / 2***or***18 / 2 scores 1 mark**provided no subsequent step*

2

- (c) (i) need a.c.

1

battery is d.c.

1

- (ii) 3 (A)

*allow 1 mark for correct substitution, ie* *$18 \times 2 = 12 \times I_s$  scores 1 mark*

**Q2.**

Marks awarded for this answer will be determined by the Quality of Written Communication (QWC) as well as the standard of the scientific response. Examiners should also apply a 'best-fit' approach to the marking.

**0 marks**

No relevant / correct content.

**Level 1 (1–2 marks)**

**Either** there is an attempt at a description of the construction of a transformer

**or**

a correct statement of the effect of one type of transformer on the input p.d.

**Level 2 (3–4 marks)**

There is a description of the construction of a transformer

**and**

a correct statement of the effect of one type of transformer on the input p.d.

**Level 3 (5–6 marks)**

There is a clear description of the construction of a transformer

**and**

there is a correct description of how transformers affect the input p.d.

**details of construction:**

*extra information*

a (laminated) core

core is made from a magnetic material / iron

2 coils

the coils are made from an electrical conductor / copper

the coils are covered in plastic / insulation

the coils are (usually) on opposite sides

step-up transformer has more turns on secondary coil than (its) primary (or vice versa)

step-down transformer has fewer turns on secondary coil than (its) primary (or vice versa)

**effect on input p.d. :**

step-up transformer, the output p.d. is greater (than the input p.d.)

*accept voltage for p.d.*

step-down transformer, the output p.d. is lower (than the input p.d.)