


Name of the Student: _____

Max. Marks : 18 Marks

Time : 18 Minutes

Mark Schemes

Q1.

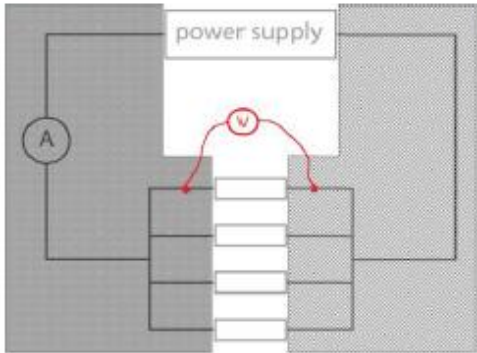Question	Answer	Additional guidance	Mark
(i)	voltmeter in parallel with resistors (1)	 <p>one voltmeter connection in each shaded region</p>	(1) AO1.2
Question	Answer	Additional guidance	Mark
(ii)	36(.4) (mA) (1)	<p>allow 36 to 37 inclusive</p> <p>may be seen in table in Figure 12</p>	(1) AO3.2

Question	Answer	Additional guidance	Mark
(iii)	<p>substitution into $V = IR$ (1)</p> <p>$6(.00) = 9.1 (\times 10^{-3}) \times R$</p> <p>rearrangement (1)</p> <p>$(R =) \frac{6(.00)}{9.1 (\times 10^{-3})}$</p>	<p>allow substitution and rearrangement in either order</p> <p>accept 18.2/2 or 27.3/3 or (36 to 37)/4 in place of 9.1</p> <p>allow substitution of correct values into a visible, incorrectly rearranged algebraic equation for this mark only</p> <p>$(R =) \frac{V}{I}$</p>	(3) AO2.1

	<p>evaluation (1)</p> <p>660 (Ω)</p>	<p>allow values that round to 660 e.g. 659.3</p> <p>award full marks for the correct answer without working.</p> <p>value rounding to 660 to any other power of 10 scores 2 marks</p>	
--	--	---	--

Question	Answer	Additional guidance	Mark
(iv)	<p>an explanation linking:</p> <p>(total) resistance increases (1)</p>		(3) AO3.2

	<p>(because) current decreases (1)</p> <p>(and) voltage stays the same (1)</p>	<p>fewer paths for the current</p> <p>resistance calculations supporting increasing resistance</p>	
--	--	--	--

Q2.

Question	Answer	Additional guidance	Mark
	substitution (1) (current =) $\frac{1.2}{4(0)}$ evaluation (1) (current =) 0.3(0) (A)	award full marks for the correct answer without working	(2) AO2.2

Q3.

Question number	Answer	Additional guidance	Mark
	substitution into $P = V \times I$ (1) $2600 = 230 \times I$ rearrangement (1) $I = P \div V$ evaluation (1) 11 (A)	Substitution and re-arrangement in either order $I = 2600 \div 230$ for 2 marks allow answers that round to 11 award full marks for correct answer without working allow $I = 2.6 \div 230$ for 1 mark allow 0.011 (A) for 2 marks max if no other marks scored, award 1 mark for 2.6 kW = 2600 W	(3)

Q4.

Question number	Answer	Additional guidance	Mark
i	<p>substitution (1)</p> $(I = \frac{P}{V}) = \frac{1.9 \times 10^3}{230} \text{ (1)}$ <p>evaluation (1)</p> <p>8.3 (A)</p>	<p>8.3 / 8.26 (A)</p> <p>award full marks for correct answer without working</p> <p>award one mark for $8.26 \times 10^{-3} / 0.0083$</p>	(2) AO2

Question number	Answer	Additional guidance	Mark
ii	<p>choice and substitution (1)</p> $E = I \times V \times t$ $= 7.4 \times 230 \times 120$ <p>evaluation (1)</p> <p>200000 (J)</p>	<p>accept 204000 / 204240</p> <p>award full marks for correct answer without working</p> <p>award 1 mark for 3400 / 3404 (J) (using 2 minutes as time)</p>	(2) AO2

Q5.

Question Number	Answer	Additional guidance	Mark
	2.5(A)	Accept $2\frac{1}{2}$ (A)	(1)