

**Name of the Student:** \_\_\_\_\_

**Max. Marks : 18 Marks**

**Time : 18 Minutes**

Mark Schemes

Q1.

Question number	Answer	Additional guidance	Mark
	d.c. - (current) in one direction only (1)	one way	<b>(2)</b> <b>AO1</b>
	a.c. - (current) changes direction (1)	both ways	

Question number	Answer	Additional guidance	Mark
(i)	<p>A description including</p> <p>as the potential difference (voltage) increases so does the current (1)</p> <p>idea of gradient of graph decreasing as V increases (1)</p>	<p>positive correlation</p> <p>at a decreasing rate</p> <p>non-linear</p> <p>not directly proportional</p>	(2) AO3

Question number	Answer	Additional guidance	Mark									
(ii)	<p>Award one mark for each row of the table</p> <table><tr><td></td><td>voltage V</td><td>current in mA</td></tr><tr><td>point P</td><td>1(.00)</td><td>20</td></tr><tr><td>point Q</td><td>3.4 ±0.1</td><td>43 ±1</td></tr></table>		voltage V	current in mA	point P	1(.00)	20	point Q	3.4 ±0.1	43 ±1	<p>ignore any units added in the boxes</p>	(2) AO2
	voltage V	current in mA										
point P	1(.00)	20										
point Q	3.4 ±0.1	43 ±1										


Question number	Answer	Additional guidance	Mark
(iii)	<p>substitution (1)</p> $(R =) \frac{4.5}{51(\times 10^{-3})}$ <p>evaluation (1)</p> <p>88.(2) (<math>\Omega</math>)</p>	<p>0.088(2) or 8.8(2) or 0.88(2) or 0.09 seen scores 1 mark</p> <p>0.088(2) k<math>\Omega</math> or 0.09 k<math>\Omega</math> scores 2 marks</p> <p>award full marks for correct answer without working</p>	(2) AO2

Question number	Answer	Additional guidance	Mark
(iv)	<p>an explanation linking any three of:</p> <p>identification of resistance increasing (1)</p> <p>heating (of the filament) (1)</p> <p>because of more collisions (1)</p> <p>of electrons (with ions / atoms / other electrons) (1)</p>	temperature increases	(3) AO1

Q3.

Question number	Answer	Additional guidance	Mark
	<p>a diagram of a circuit including <b>all</b> of the following:  power supply / cell(s) / battery,  identifiable resistance wire  an ammeter  a voltmeter (1)</p> <p>plus any <b>two</b> from  ammeter in series (1)  voltmeter in parallel (1)</p> <p>indication of tapping off / using  50cm of resistance wire (1)</p>	<p>accept symbols</p> <p>accept ohmmeter  with resistance wire  only</p> <p>ignore lamp(s) /  additional resistors</p> <p>allow ohmmeter  (across wire) instead  of ammeter and  voltmeter for 1 mark</p> <p>e.g. (crocodile) clips</p>	<p><b>(3)</b></p> <p><b>A02</b></p>

Q4.

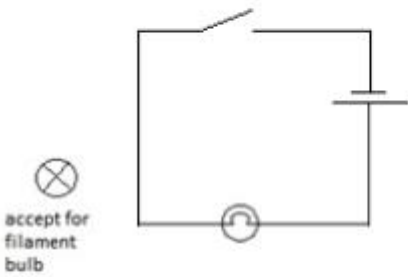Question number	Answer	Additional guidance	Mark
	<div data-bbox="379 271 788 546">  <p>accept for filament bulb</p> </div> <p data-bbox="347 562 724 680">           battery/cell symbol (1)            lamp symbol (1)            switch symbol (1)         </p> <p data-bbox="347 757 890 833">           then            complete series circuit shown (1)         </p>	<p data-bbox="1102 595 1273 714">ignore polarity of battery</p>	<p data-bbox="1318 203 1398 280">(4) AO3</p>